

EECS Laboratory


Experiment 4

Rita Abani 19244


Date : 10.02.2022

4.1. HALF WAVE RECTIFIER

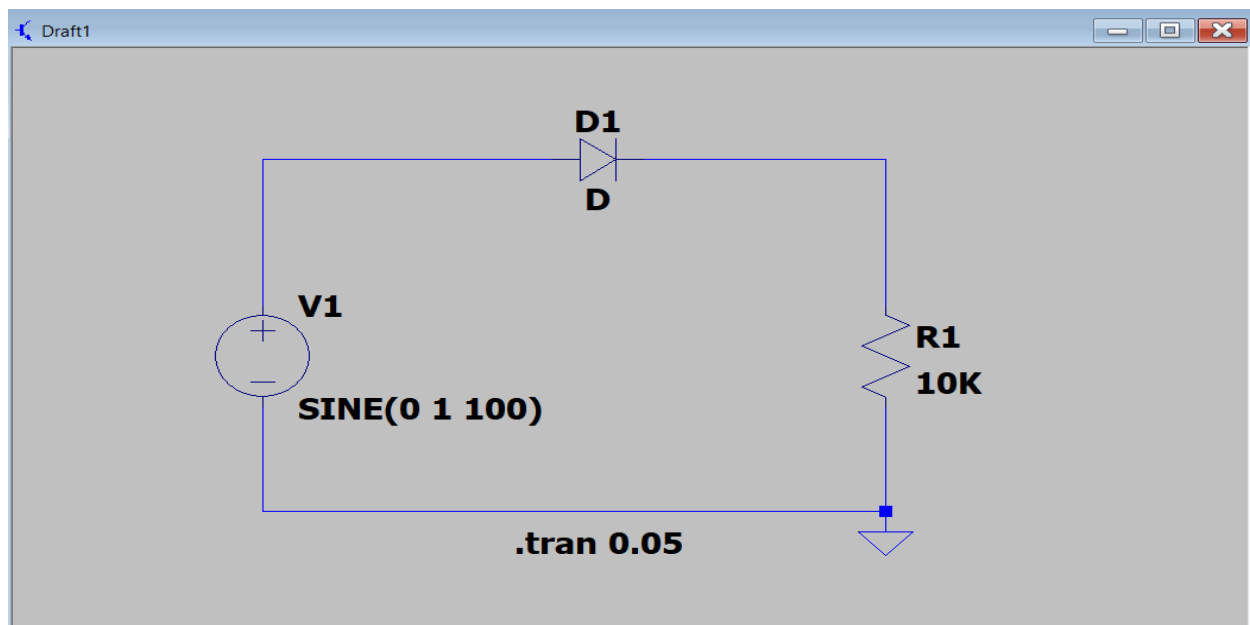
4.1.4.1 Half wave rectifier without a filter (without capacitor)




Input waveform

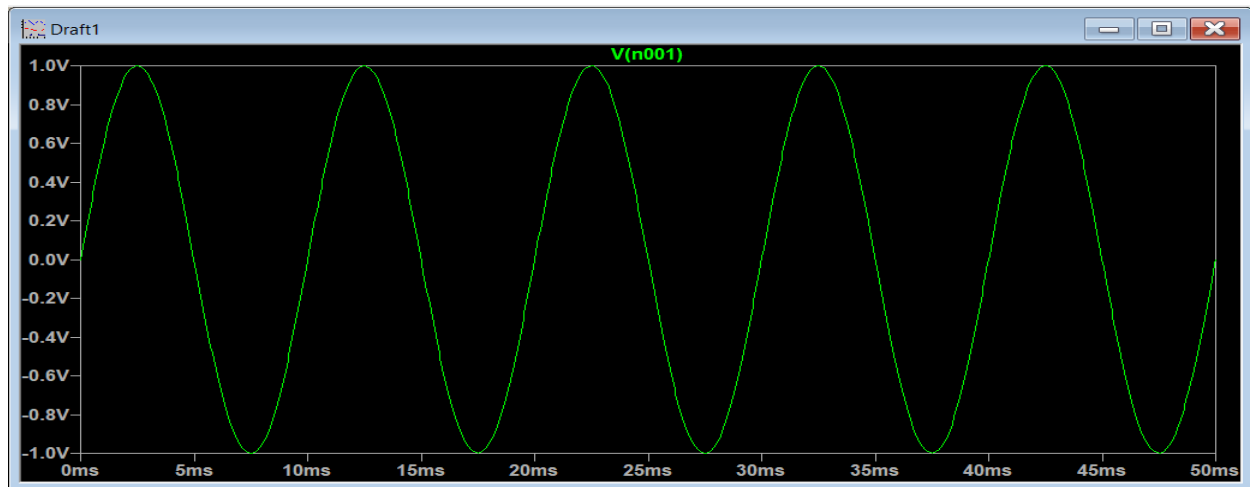


Output waveform

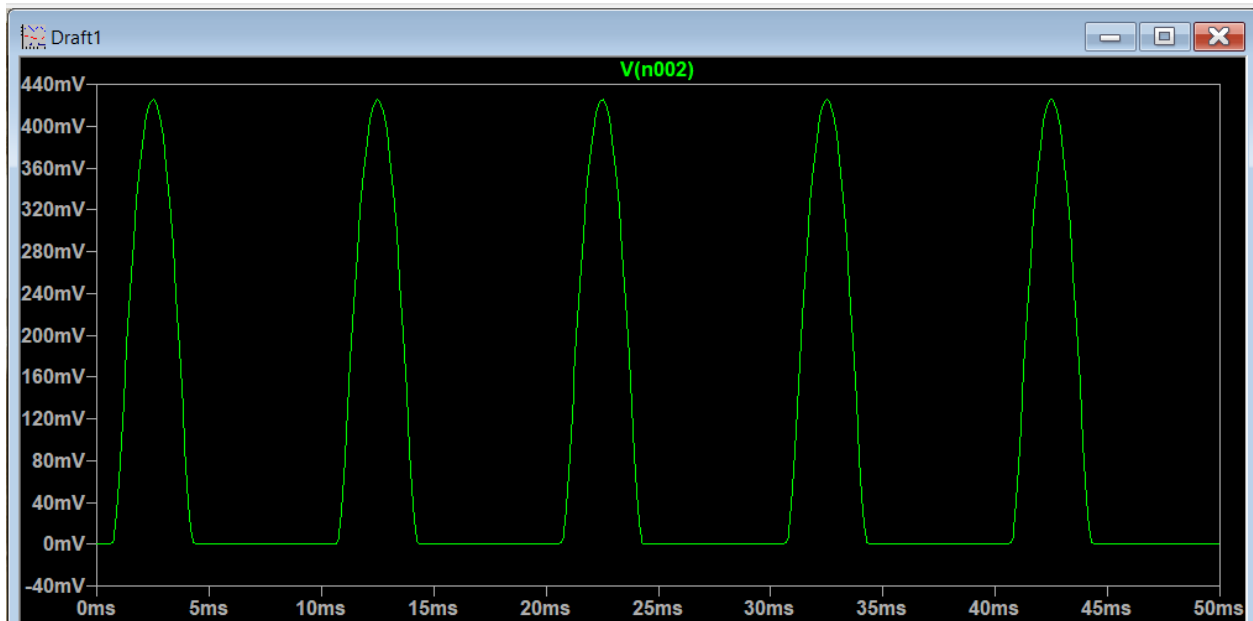

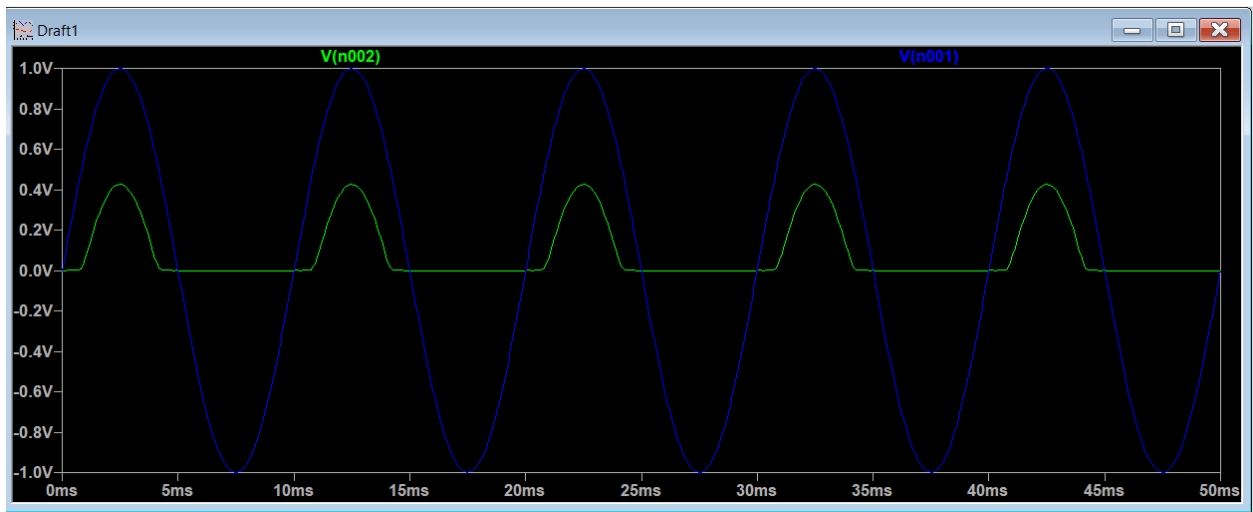
Both input and output waveforms on the same graph





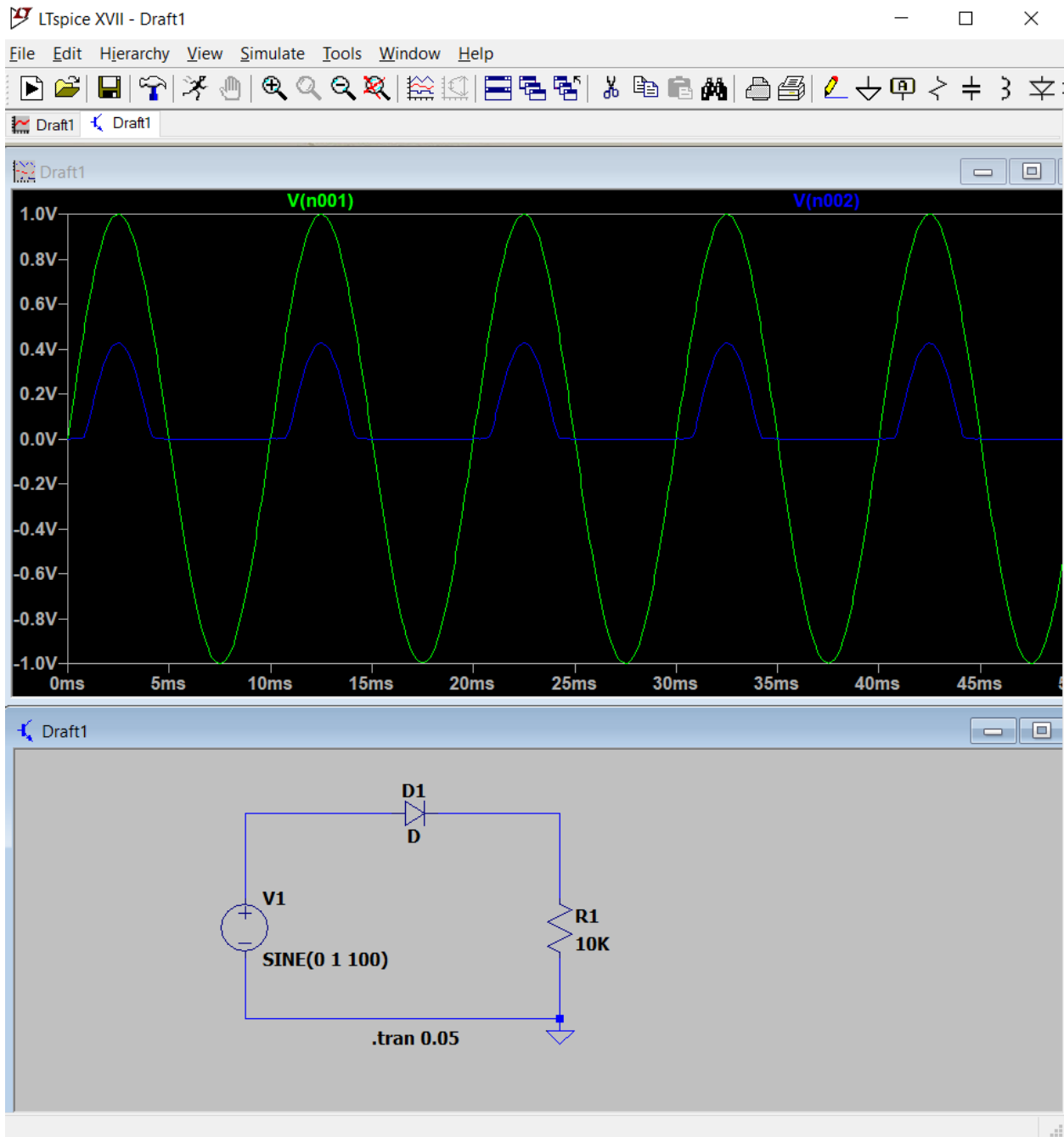

4.1.4.1 Half wave rectifier with a filter (with smoothing capacitor)


Circuit diagram


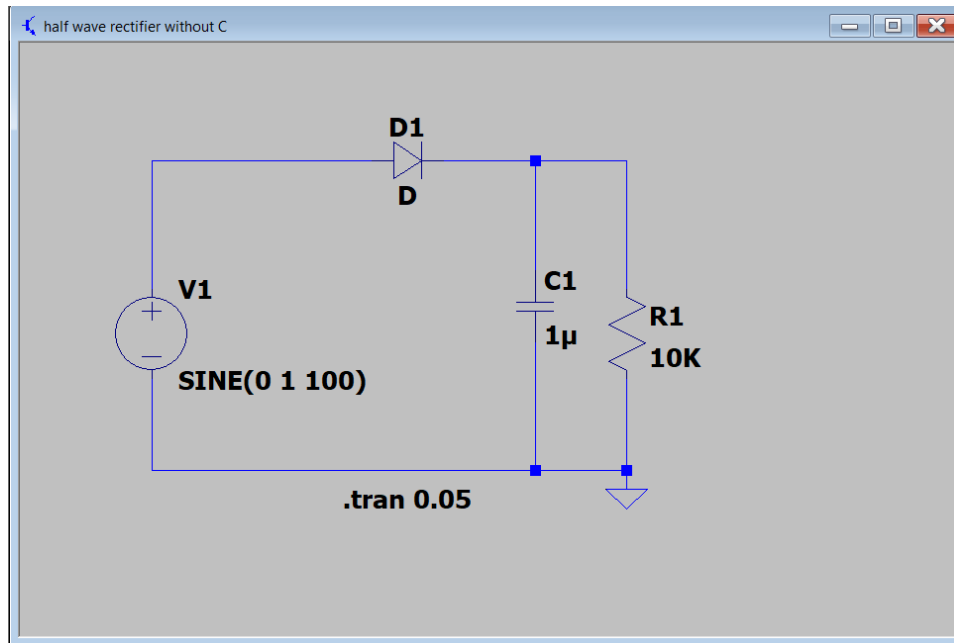


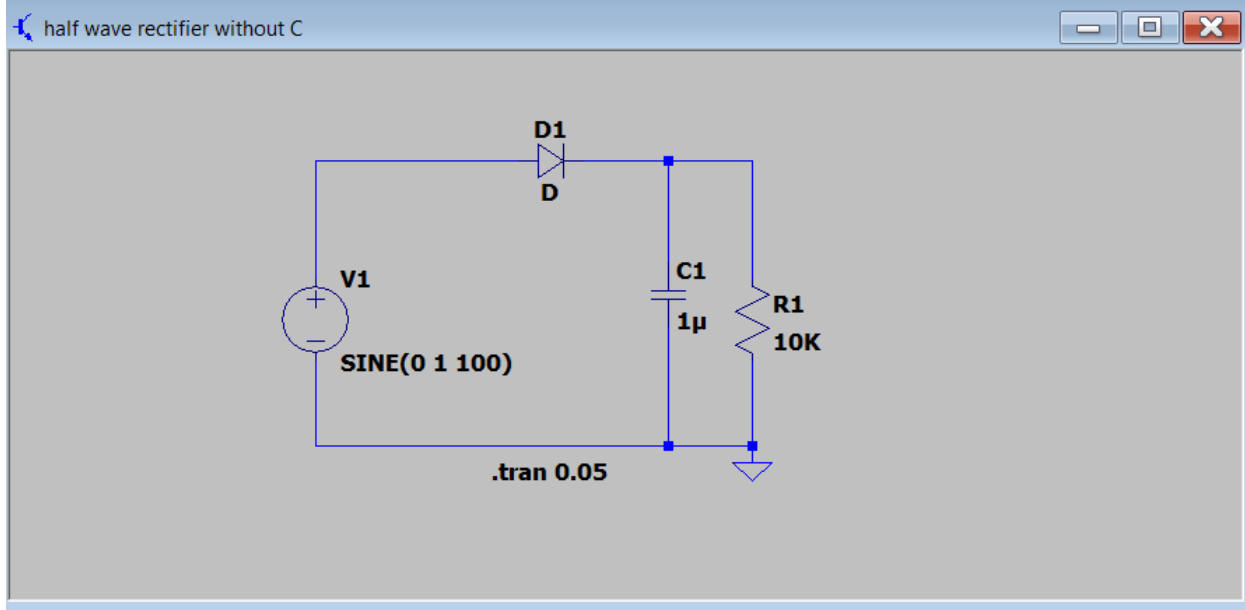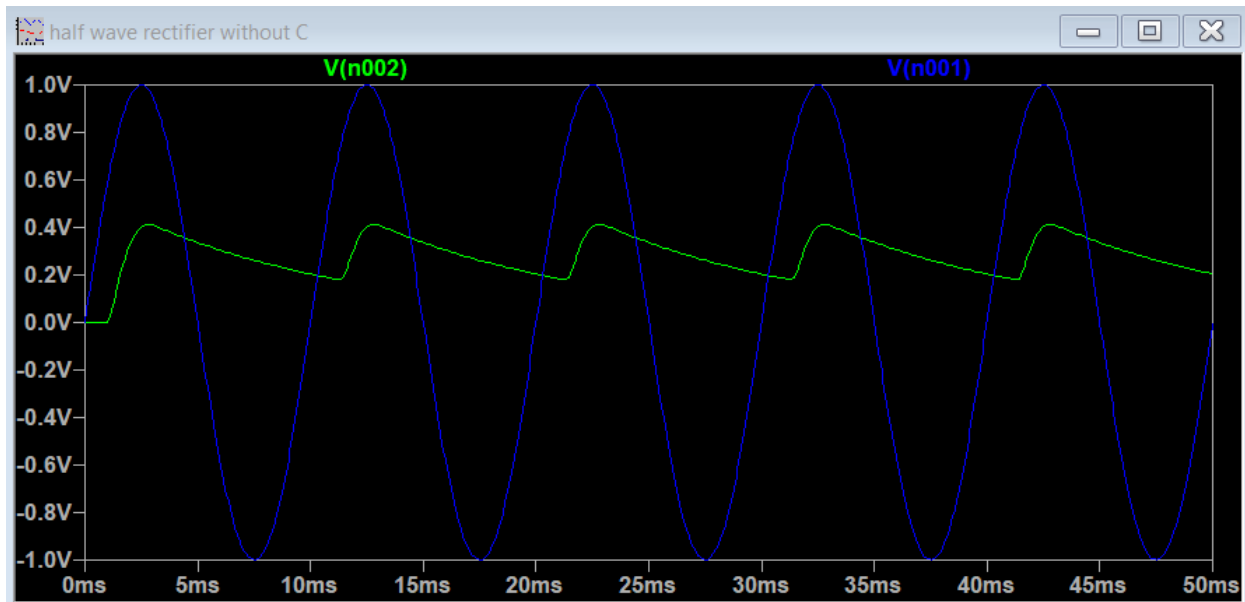




4.2. FULL WAVE RECTIFIER

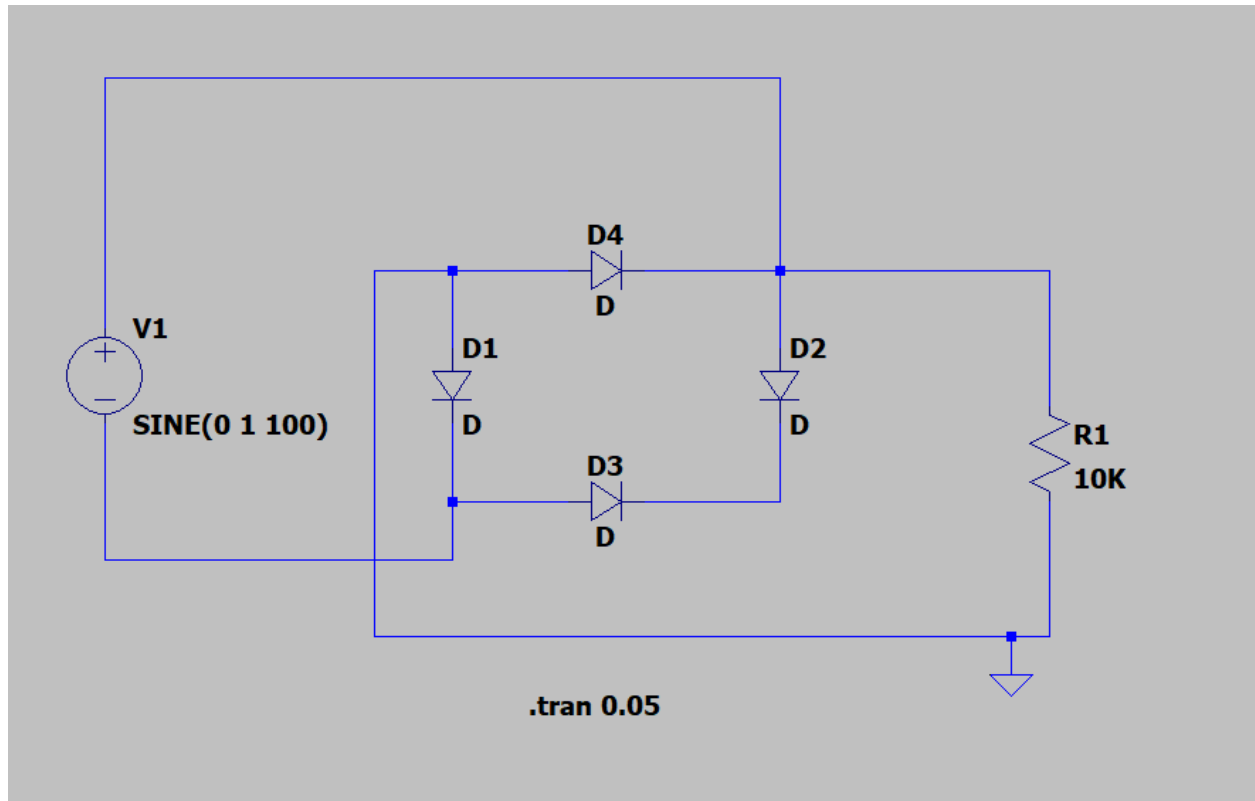4.2.1 FULL WAVE RECTIFIER WITHOUT CAPACITOR



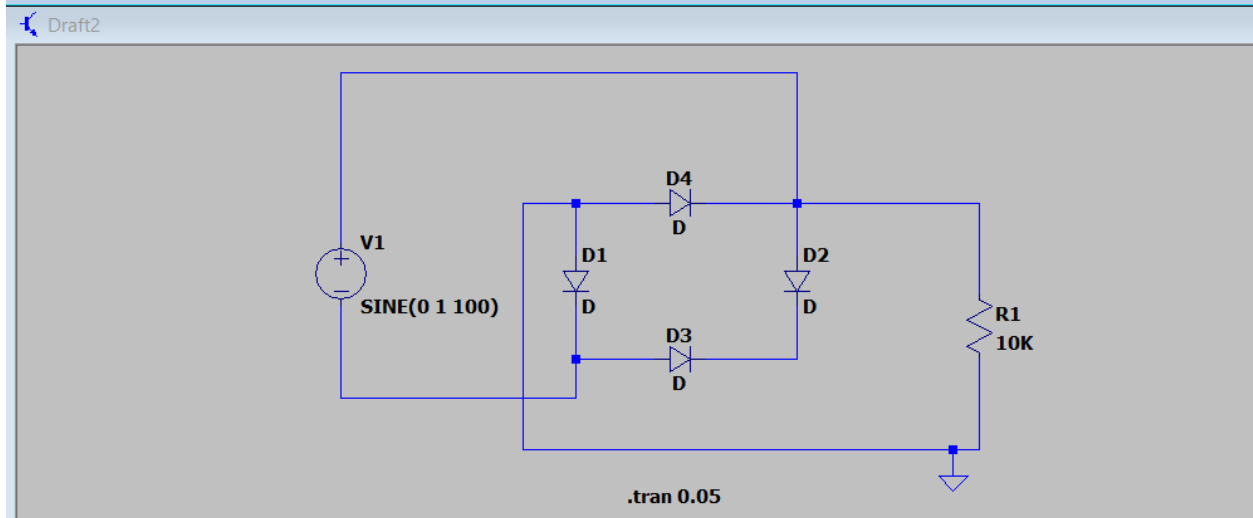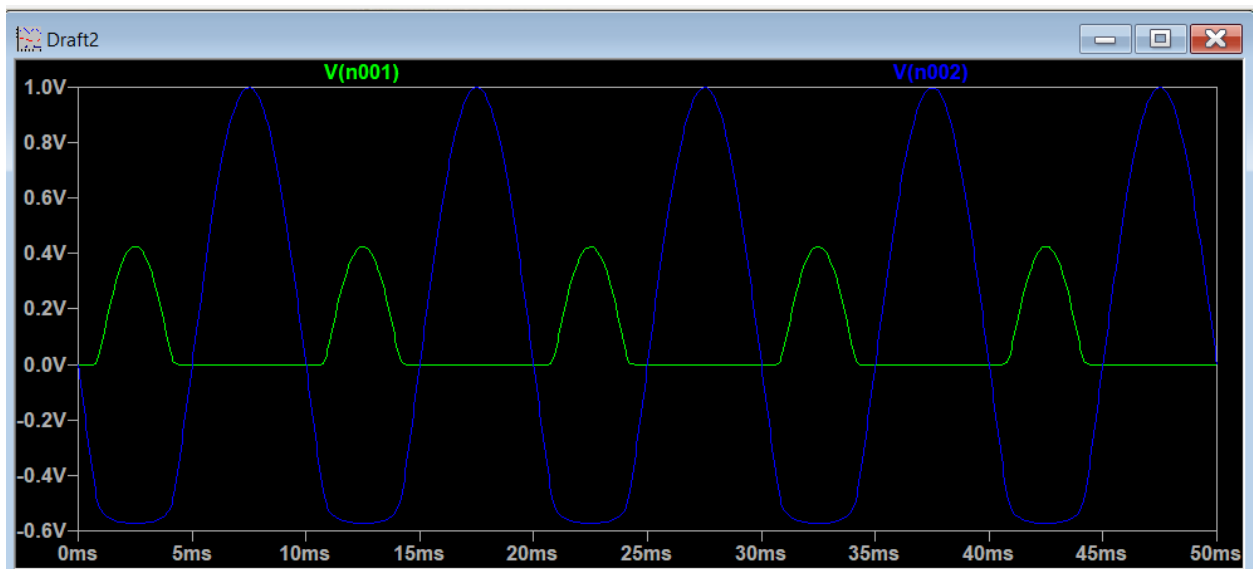

4.2.1 FULL WAVE RECTIFIER WITH CAPACITOR

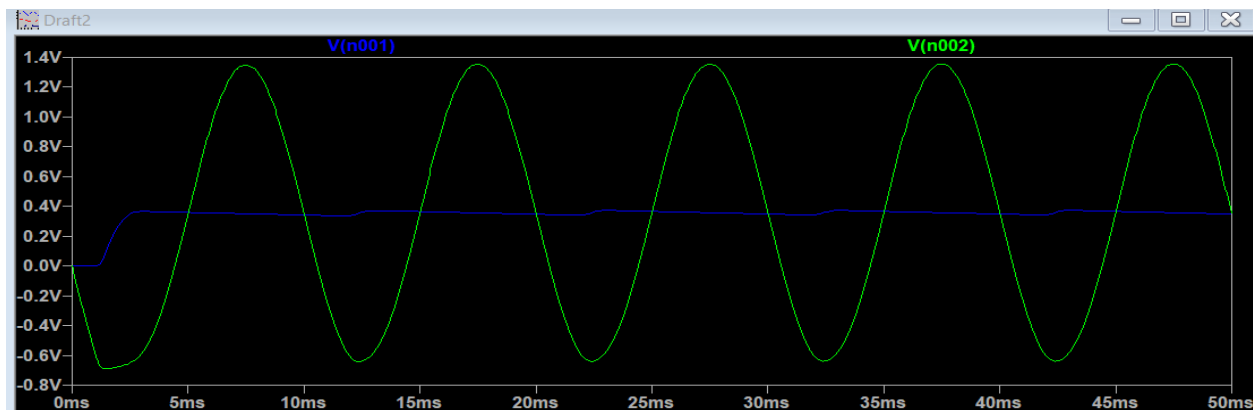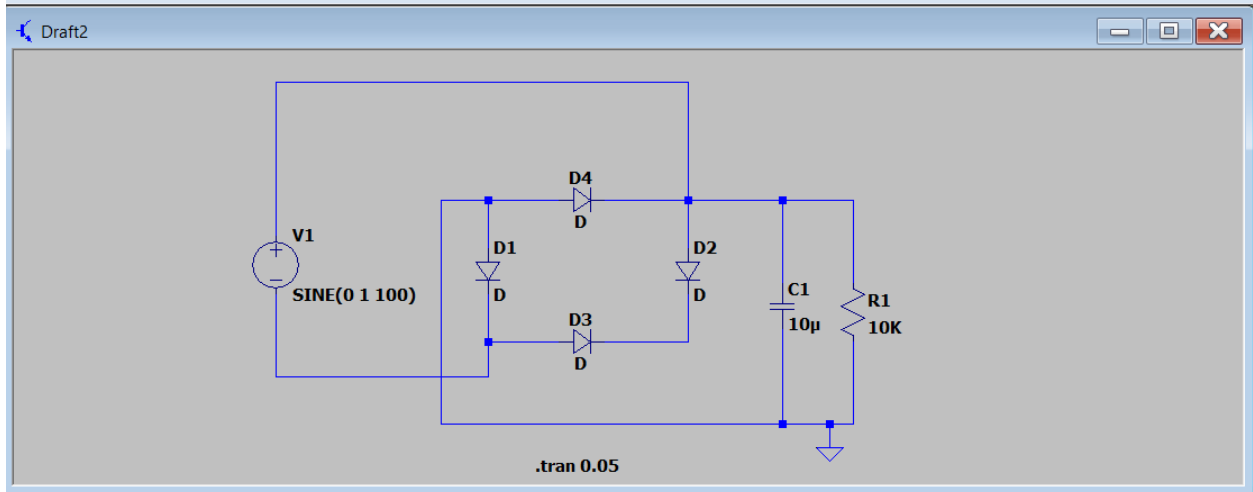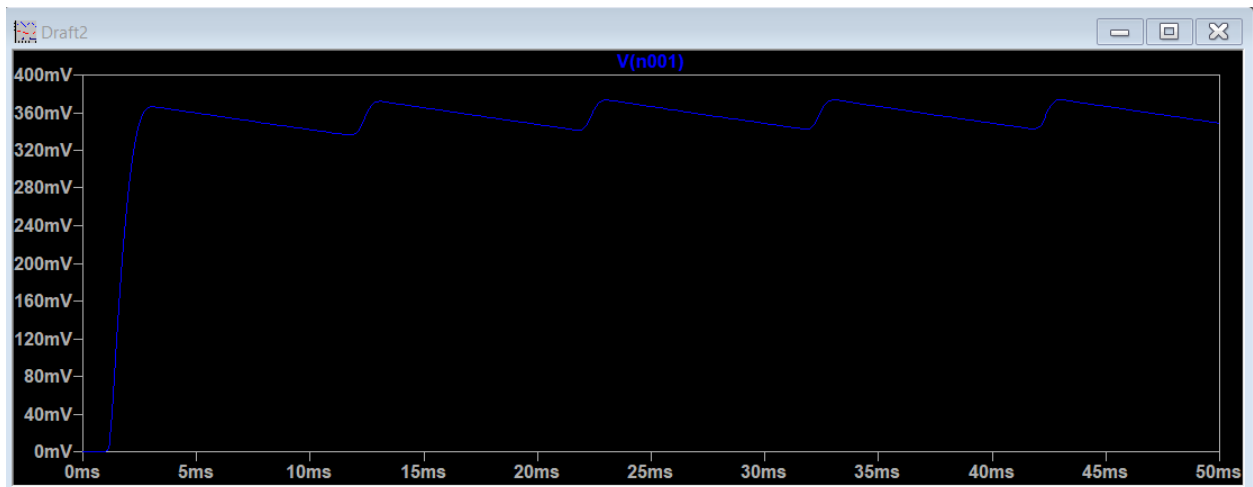

4.2.5 RIPPLE FACTOR CALCULATIONS

Rectifier without filter:

HWR	V_m	$V_{rms} = V_m / 2$	$V_{dc} = V_m / \pi$	$r = V_{r,rms} / V_{dc}$
	1V	0.5V	0.318V	1.213
FWR	V_m	$V_{rms} = V_m / \sqrt{2}$	$V_{dc} = 2V_m / \pi$	$r = V_{r,rms} / V_{dc}$
	1V	0.707	0.636	0.485

Rectifier with filter :

Type	V_m	V_{rpp}	$V_{r,rms}$	$V_{dc} = V_m - V_{rpp} / 2$	$r = V_{r,rms} / V_{dc}$
HWR	0.5V	0.236	0.0681	0.382	0.178
FWR	0.366V	31.05mV	8.96mV	351.045mV	0.025

The values for V_m , V_{rpp} have been taken from the output waveforms shown in the above snippets of LTSpice

CALCULATIONS:

1. HWR without filter:

$$\text{Ripple factor} = \sqrt{(V_{rms}/V_{dc})^2 - 1}$$

2. HWR with filter:

$$\text{Ripple factor} = V_{rms}/V_{dc}$$


3. FWR without filter:

$$\text{Ripple factor} = \sqrt{(V_{rms}/V_{dc})^2 - 1}$$


4. FWR with filter:

$$\text{Ripple factor} = V_{rms}/V_{dc}$$


4.3 CLIPPER CIRCUIT

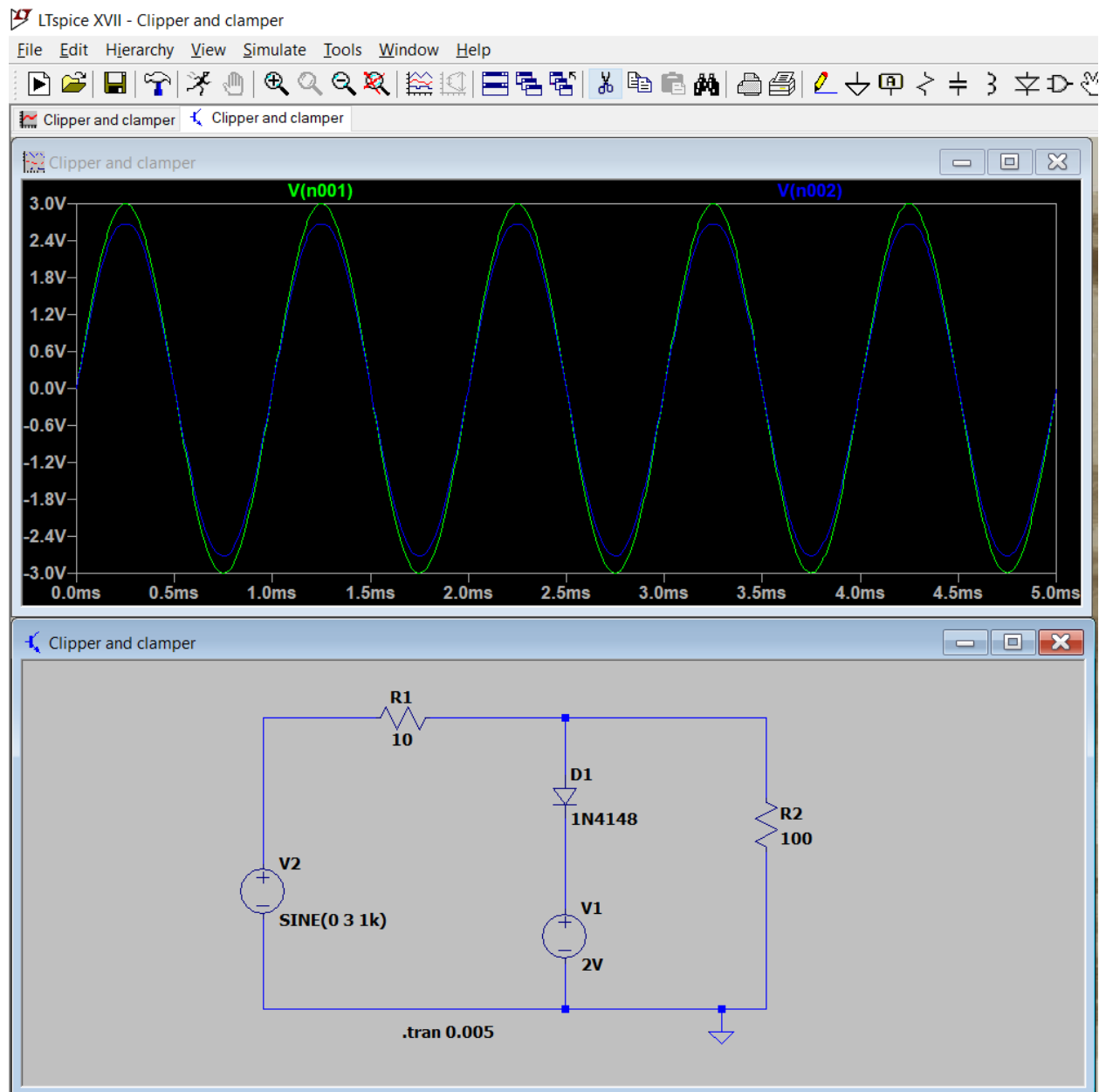

4.4. CLAMPER CIRCUIT

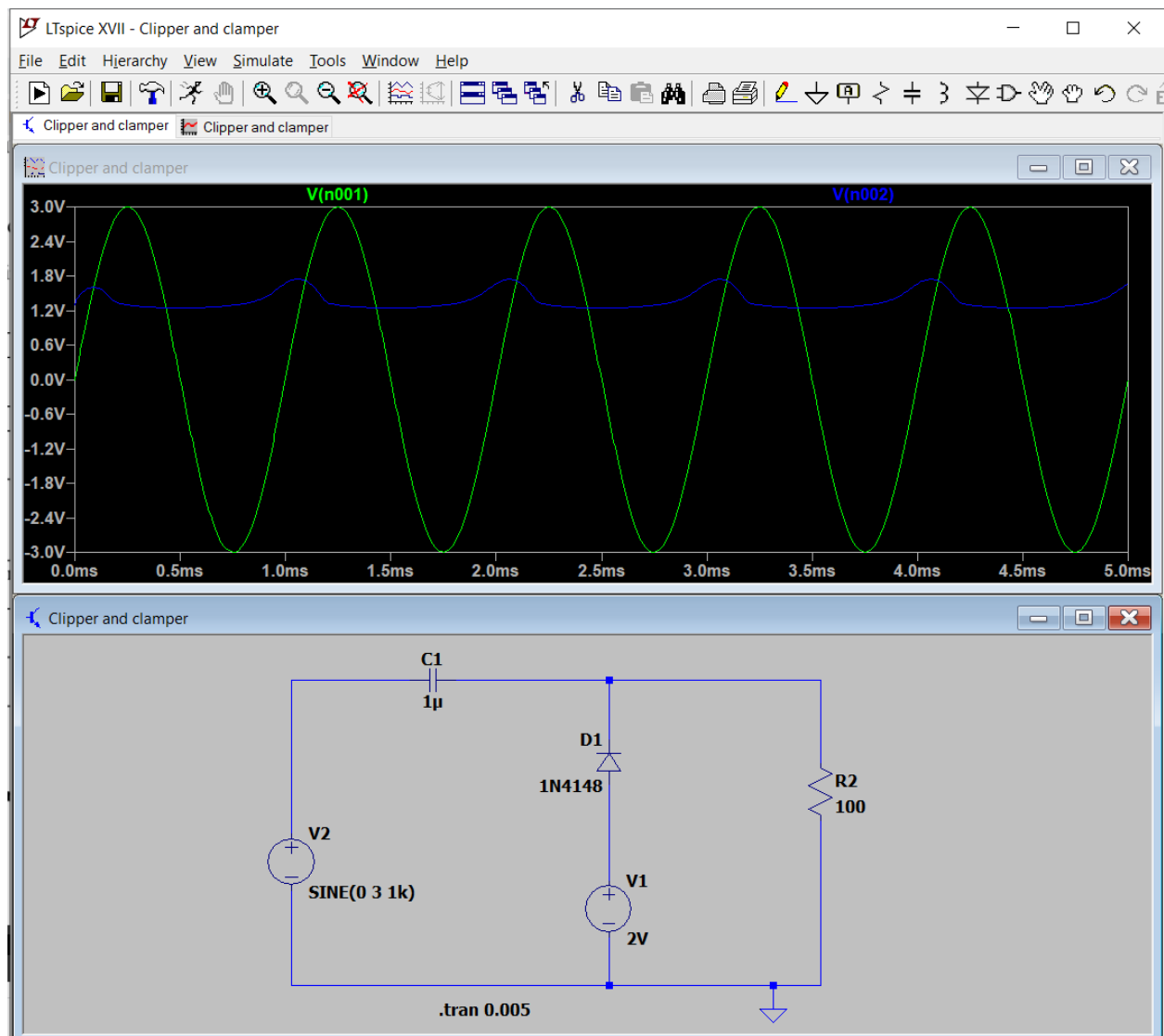


4.5 Voltage Doubler

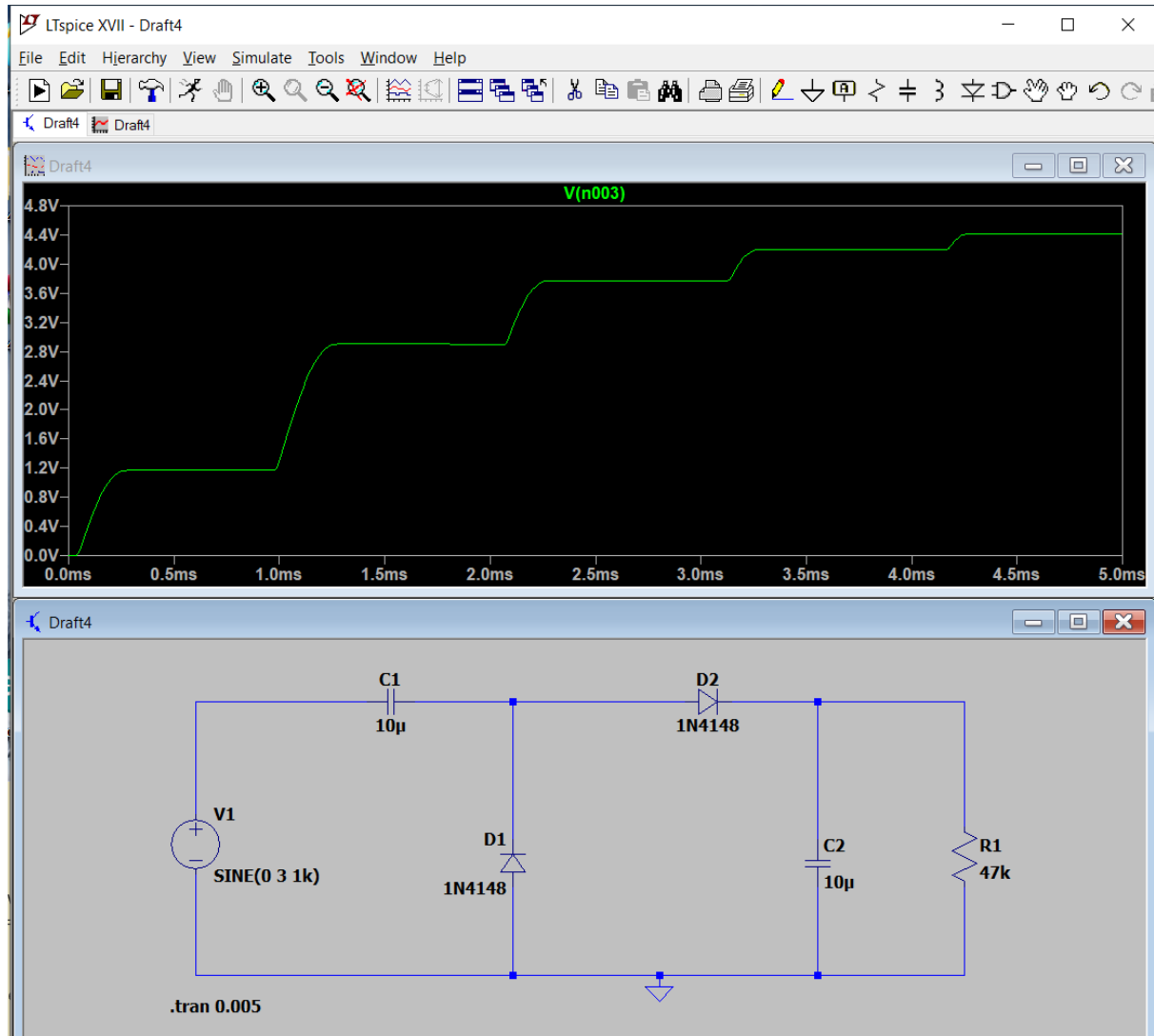


4.6 LOGIC GATES


Inverter :

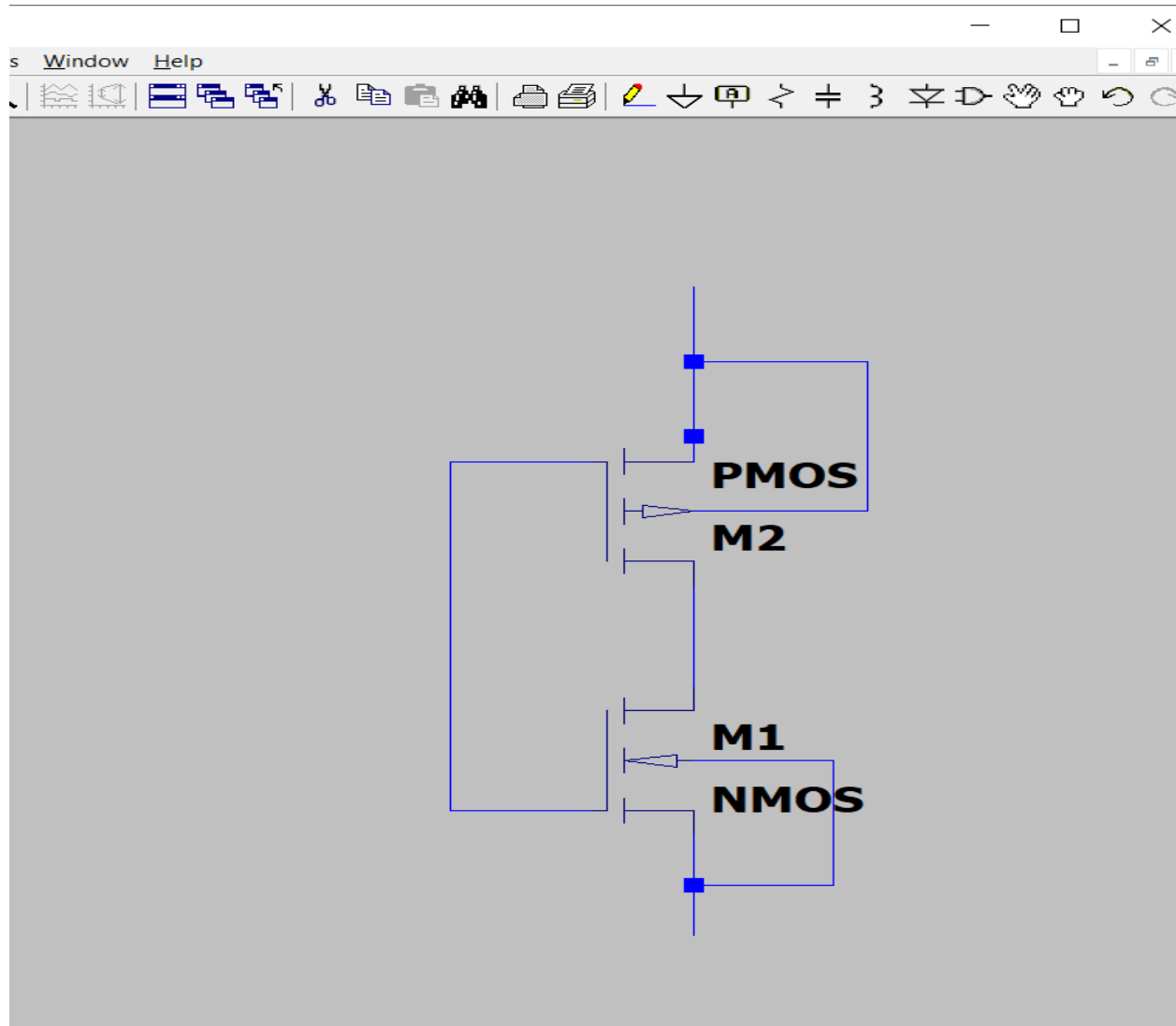


NOT Gate:

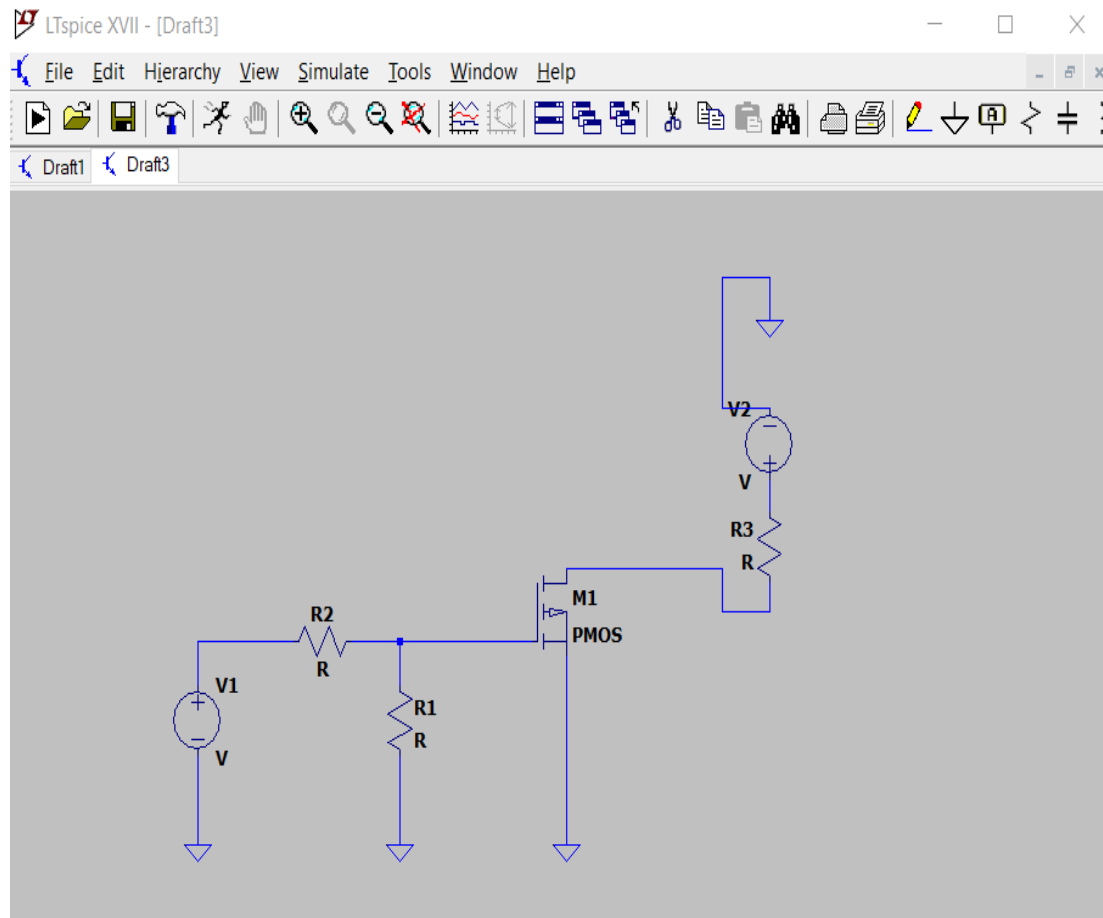


NOR GATE:

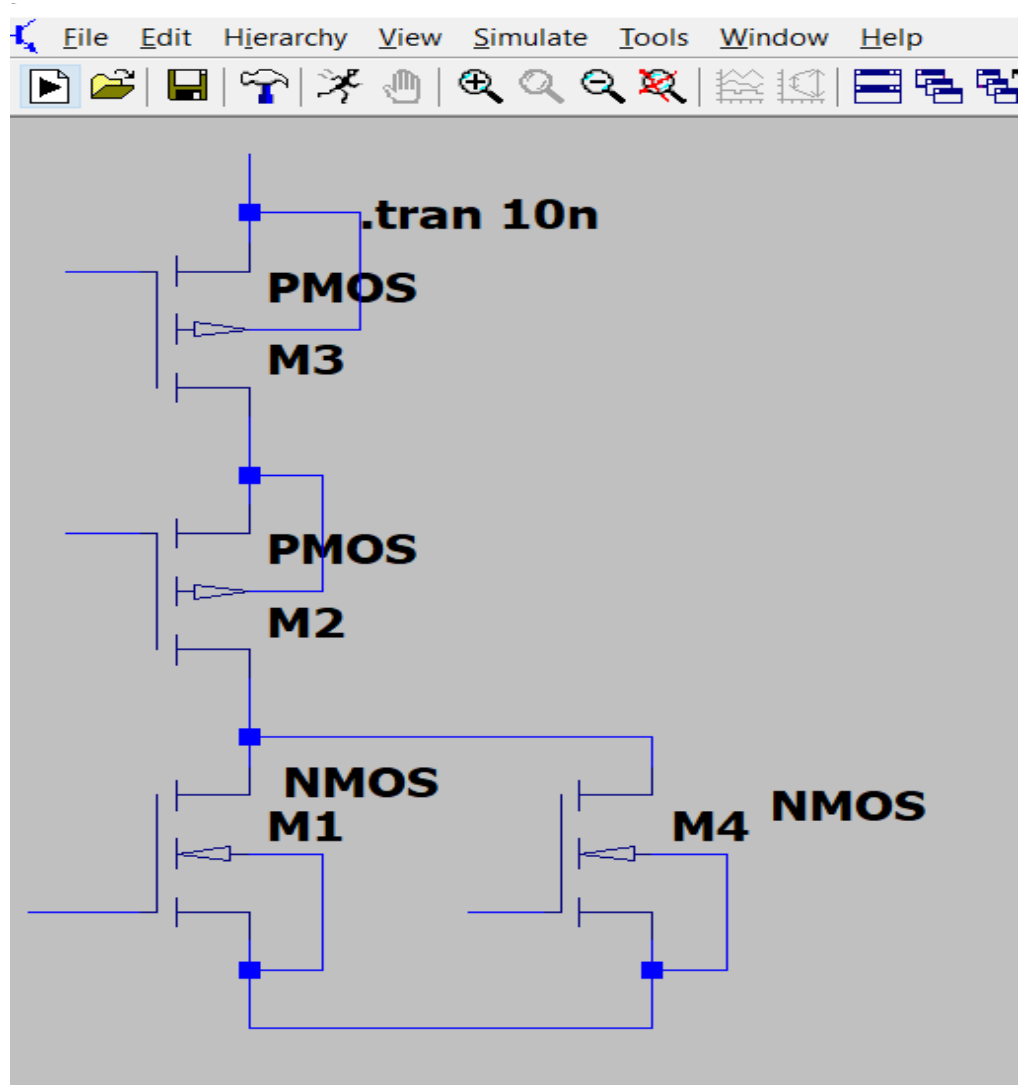

NAND Gate :

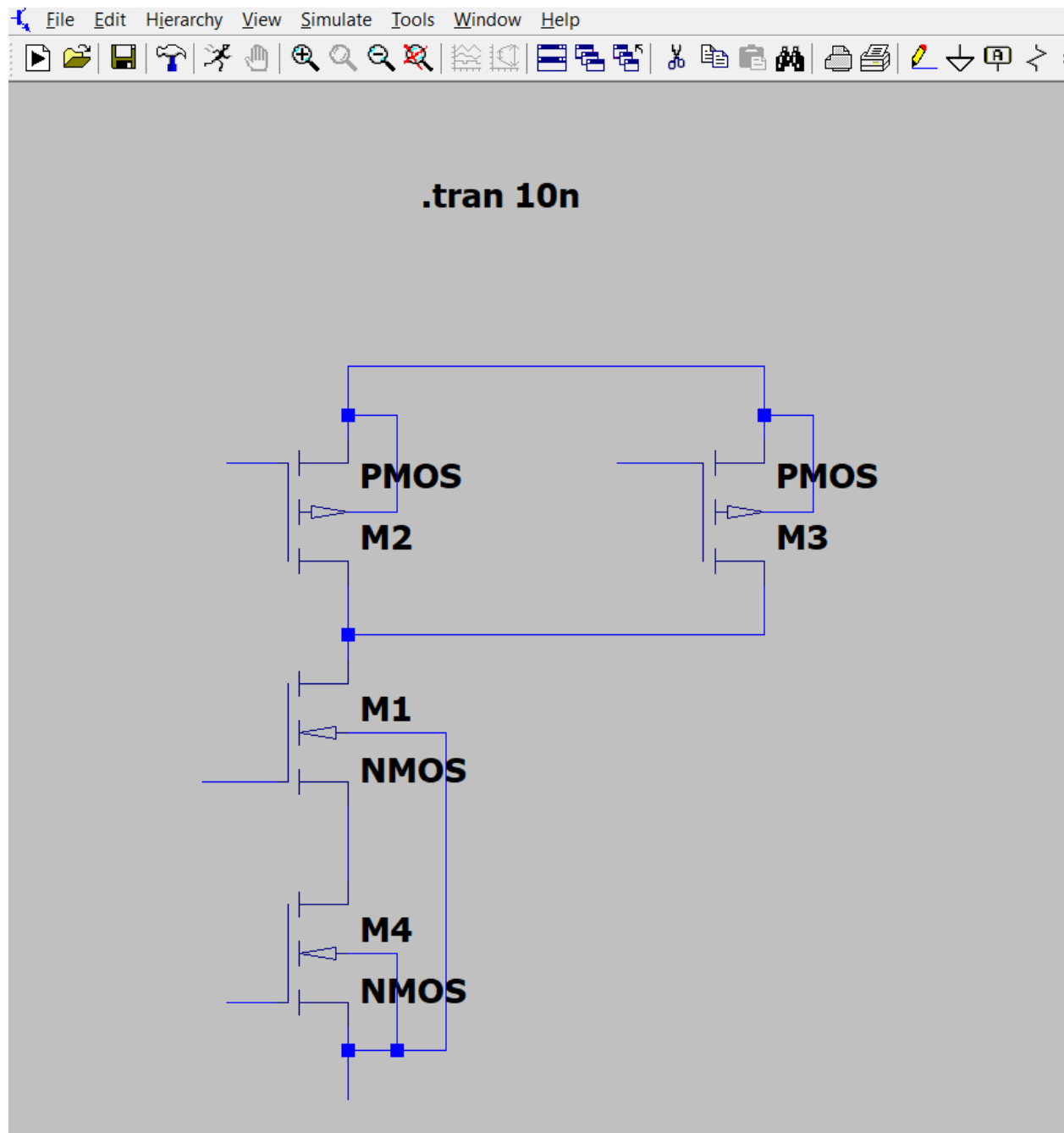

AND gate:

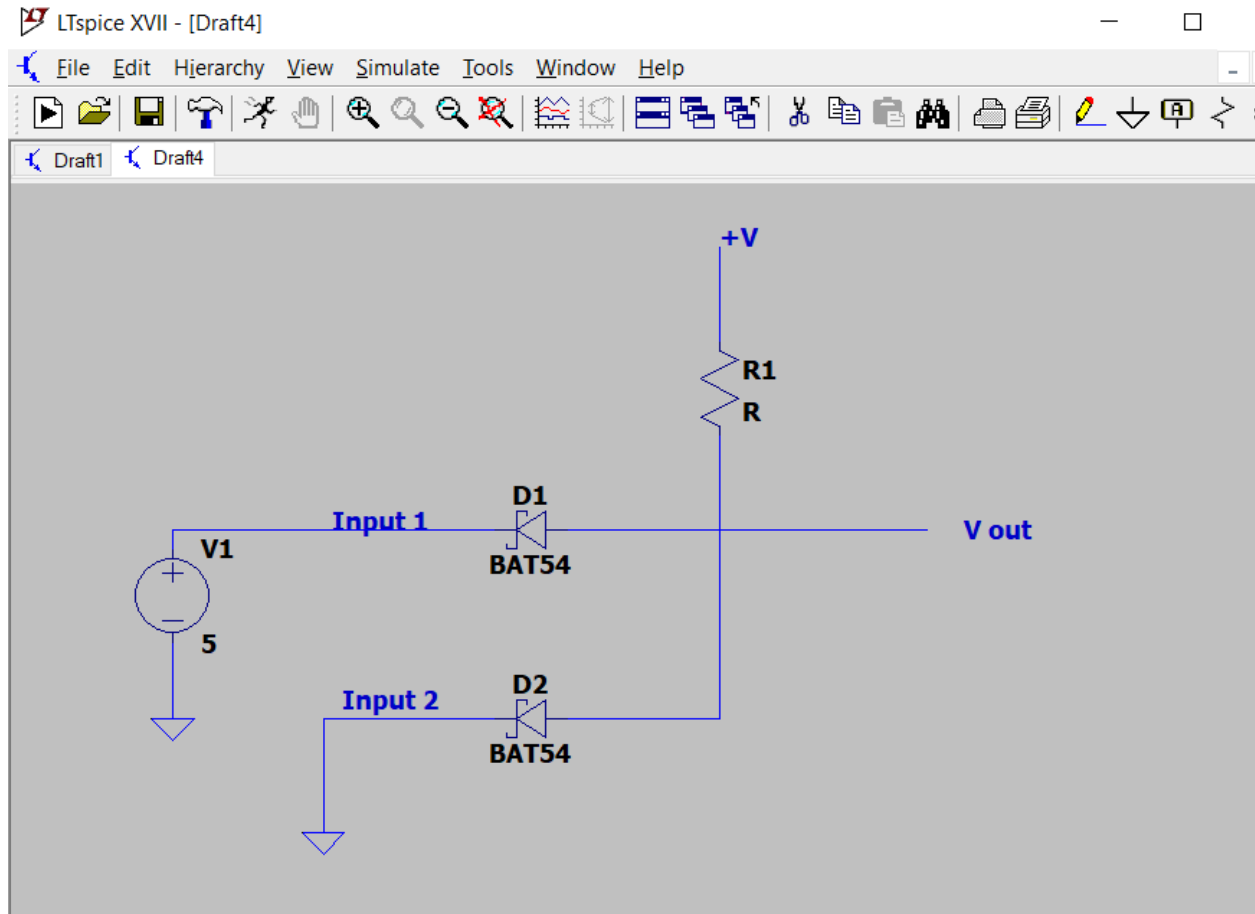

OR GATE:

