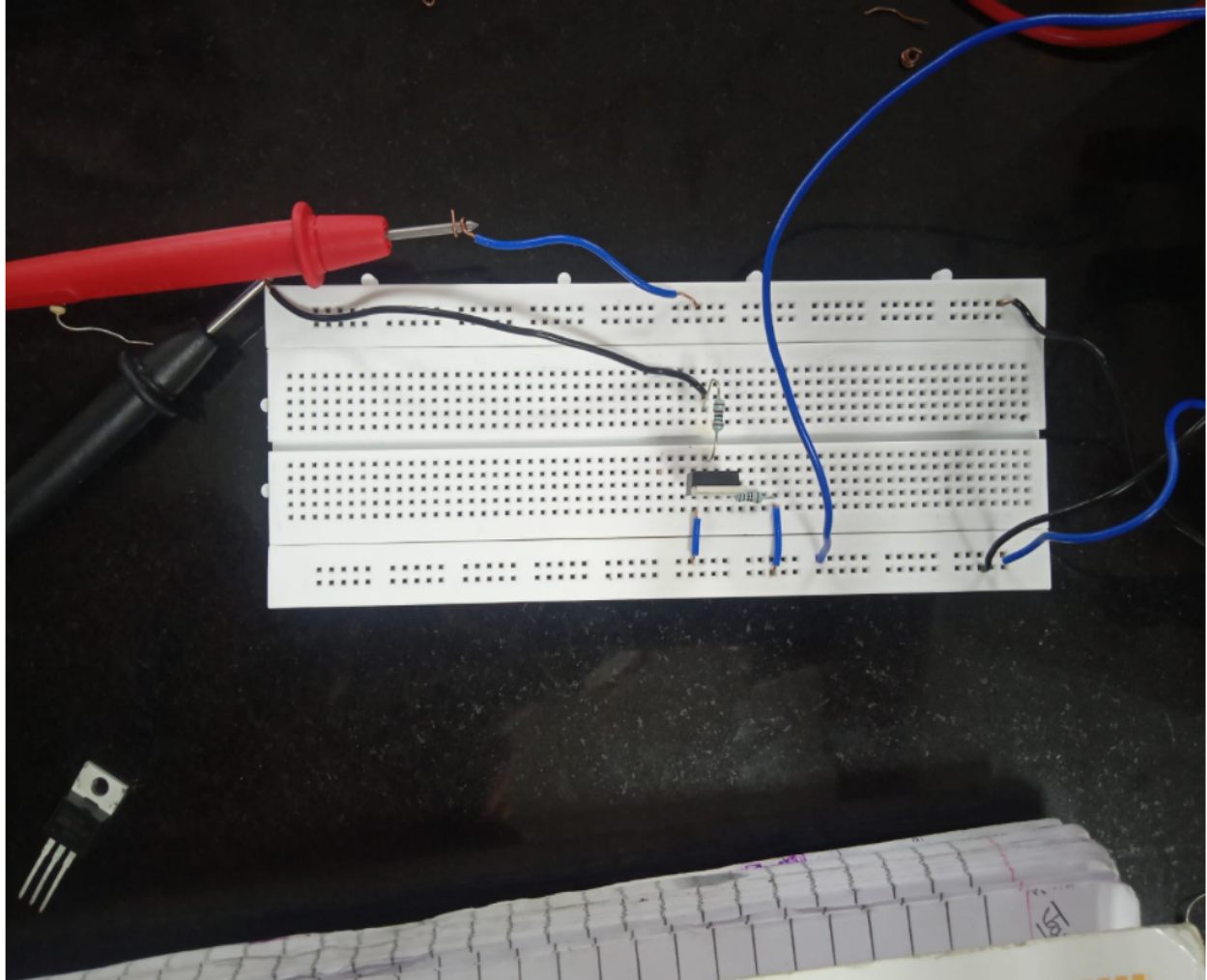


EECS Laboratory Experiment 8

Rita Abani 19244
Date : 27- 03 -2022

A few images of the experimental set-up



EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022




EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

NMOS schematic in LTSpice

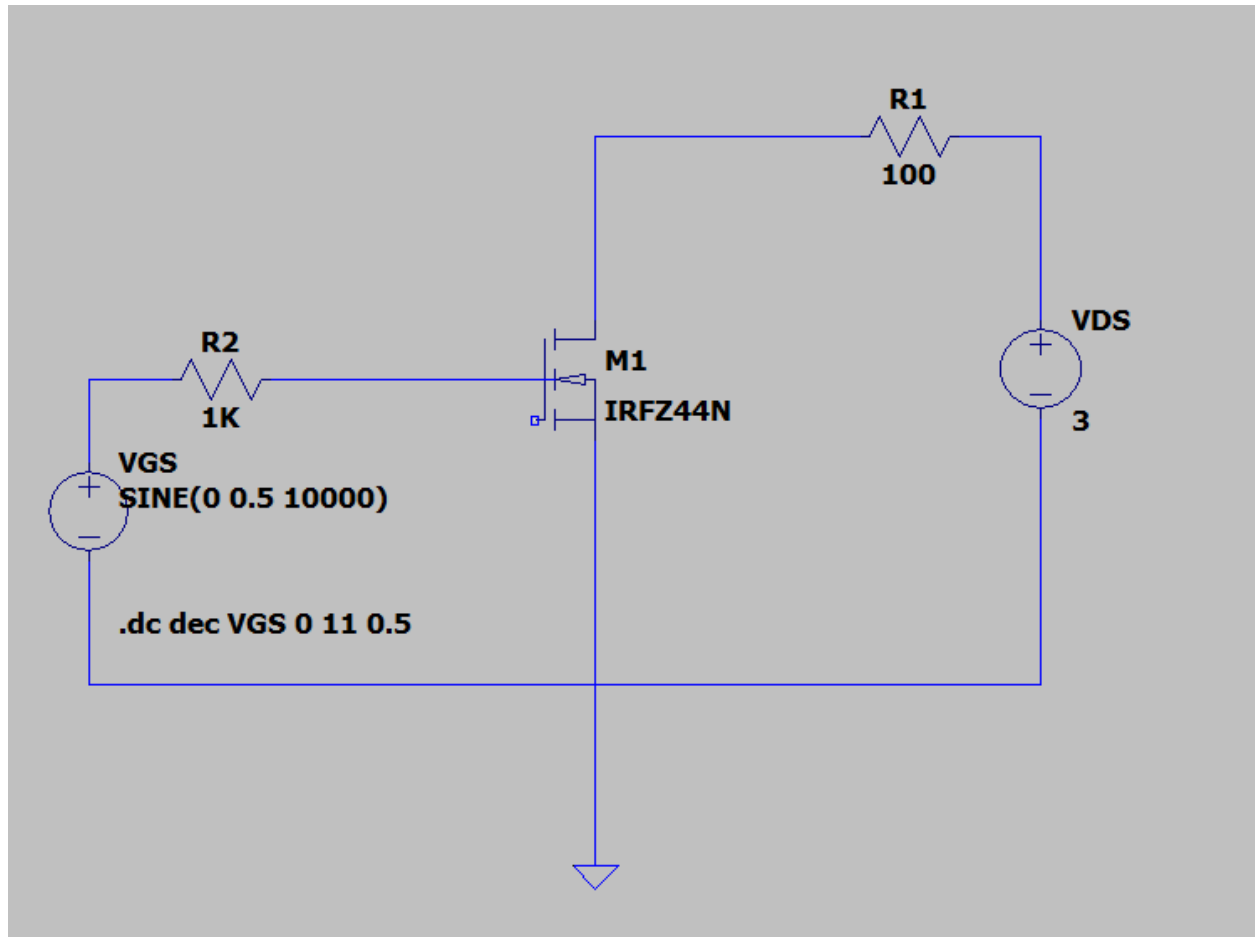


EECS Laboratory Experiment 8


Rita Abani 19244

Date : 27- 03 -2022

For $V_{DS} = 3V$

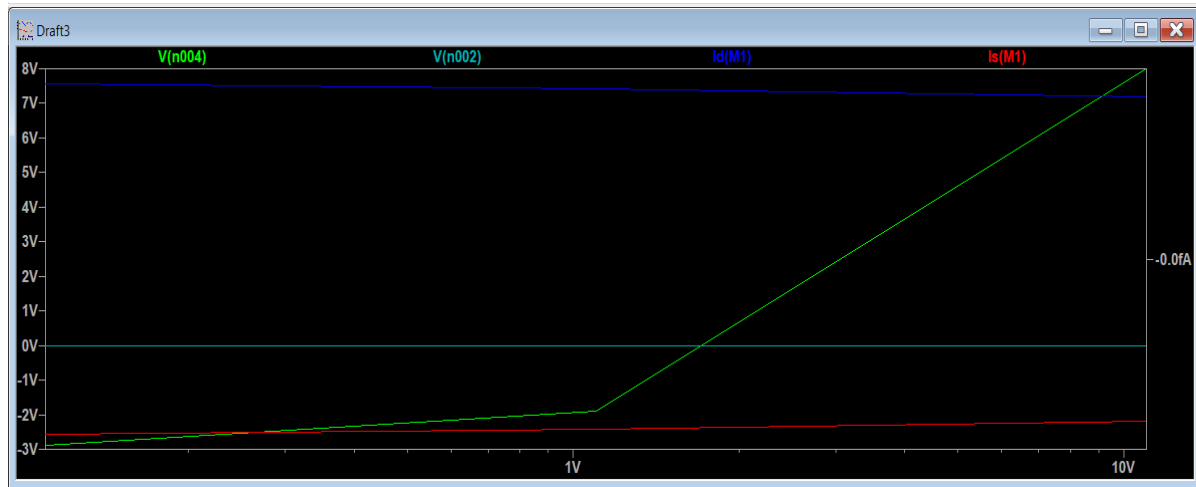

For $V_{DS} = 8V$

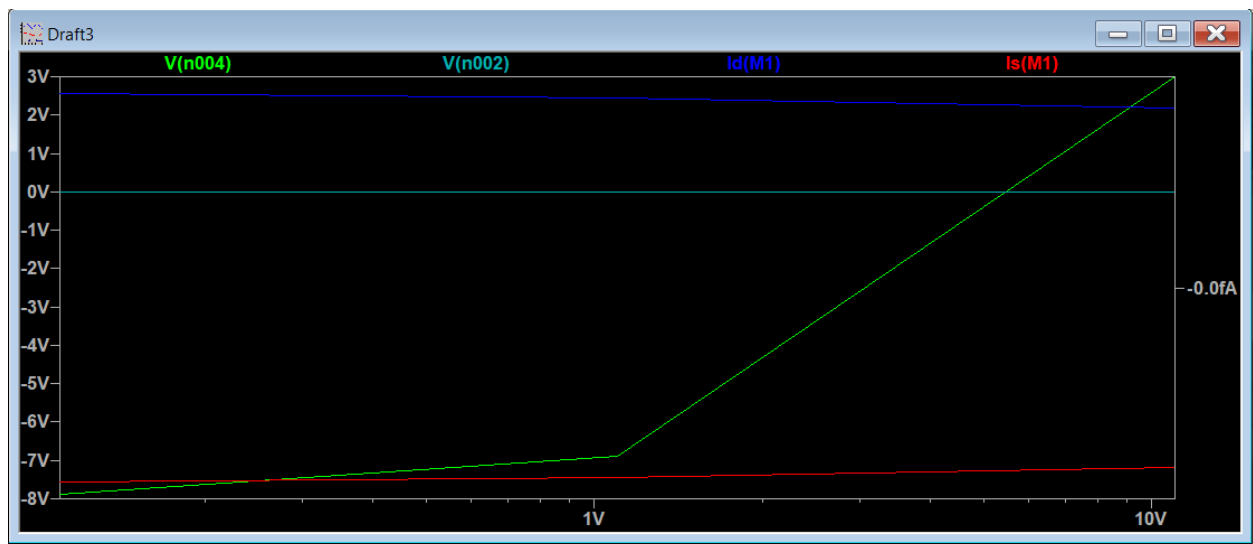


For $V_{DS} = 11V$

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

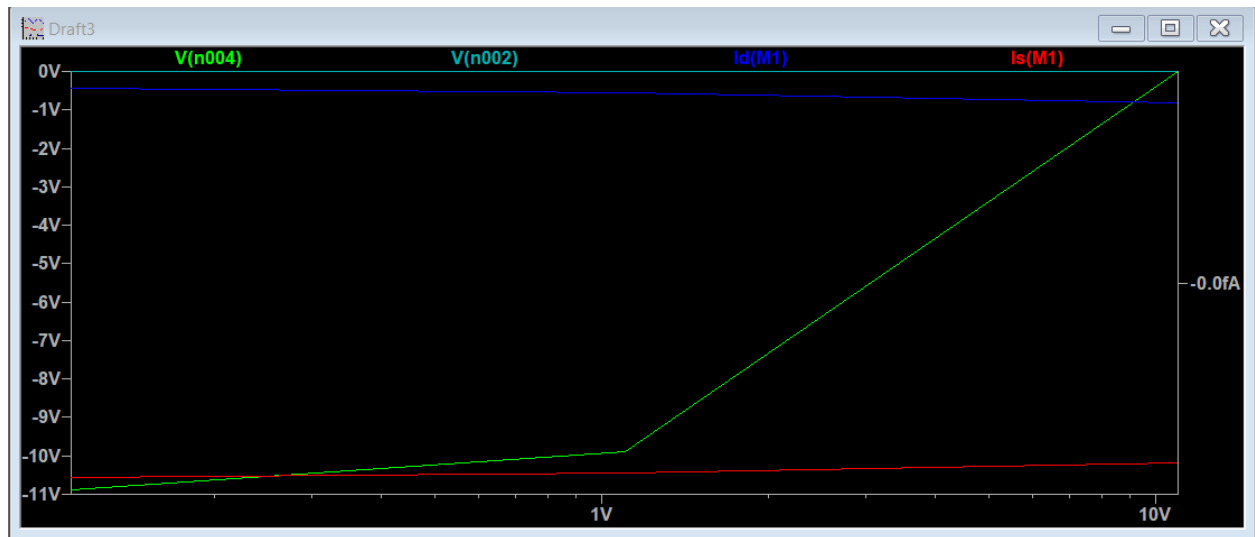

Output characteristics :




EECS Laboratory Experiment 8


Rita Abani 19244

Date : 27- 03 -2022

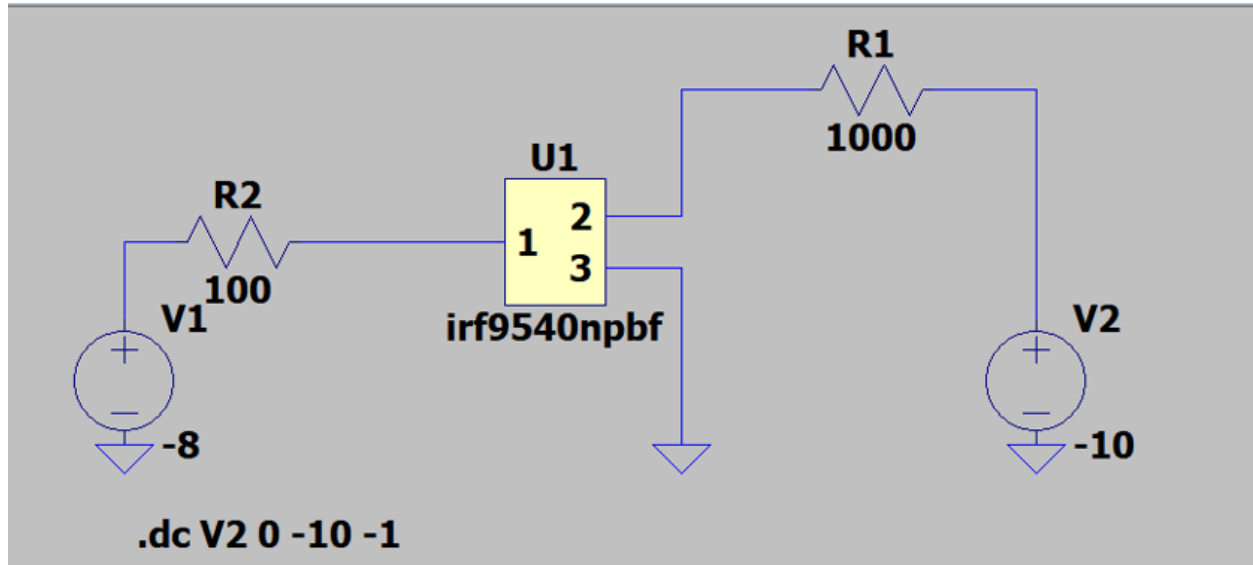LTSpice Schematic for PMOS circuit is as follows :



Transfer characteristics for PMOS:

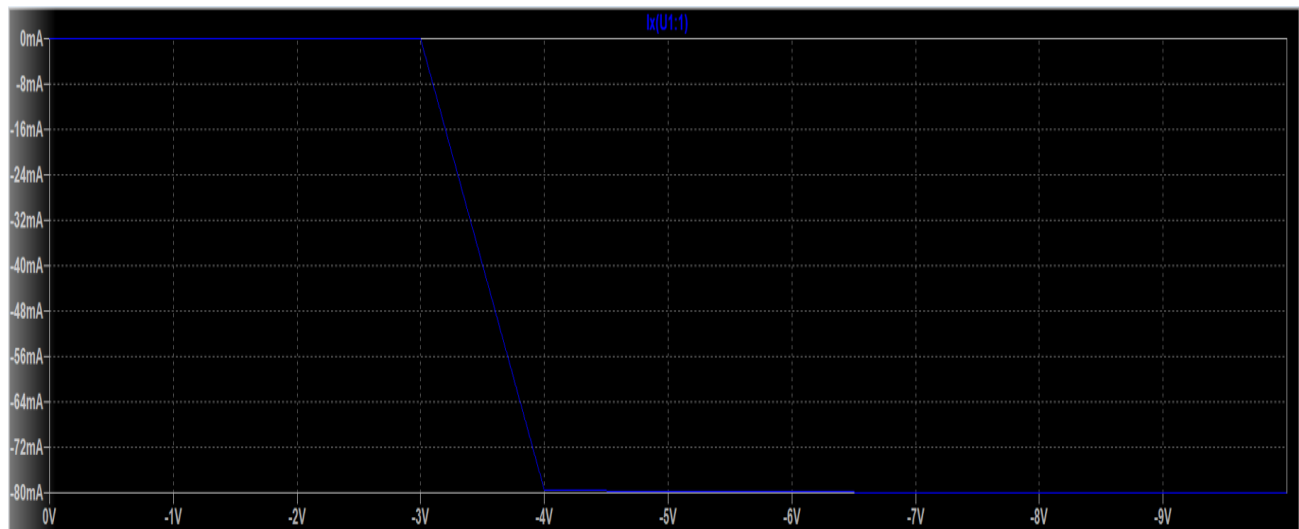

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

Experimental results (performed in the lab)

For NMOS:

TRANSFER CHARACTERISTICS


V_{GS} (V)	$V_{DS} = 8\text{ V}$	$V_{DS} = 11\text{ V}$	V_{GS} (V)	$V_{DS} = 8\text{ V}$	$V_{DS} = 11\text{ V}$
	I_D (mA)	I_D (mA)		I_D (mA)	I_D (mA)
0	0.01	0.01	6	71.8	106.1
0.5	0.01	0.01	6.5	71.8	106.2
1	0.01	0.05	7	72.3	106.2
1.5	0.01	0.01	7.5	72.4	106.3
2	0.01	0.01	8	72.6	106.4
2.5	0.20	0.61	8.5	72.8	106.0
3	13.55	18.61	9	72.7	106.3
3.5	63.6	90.9	9.5	73.1	105.6
4	70.9	104.5	10	73.3	104.6
4.5	71.9	106.1	10.5	72.9	104.9
5	71.3	106.2	11	72.7	104.5
5.5	71.1	106.1			

EECS Laboratory Experiment 8


Rita Abani 19244

Date : 27- 03 -2022

ID vs. VGS for VDS=8V

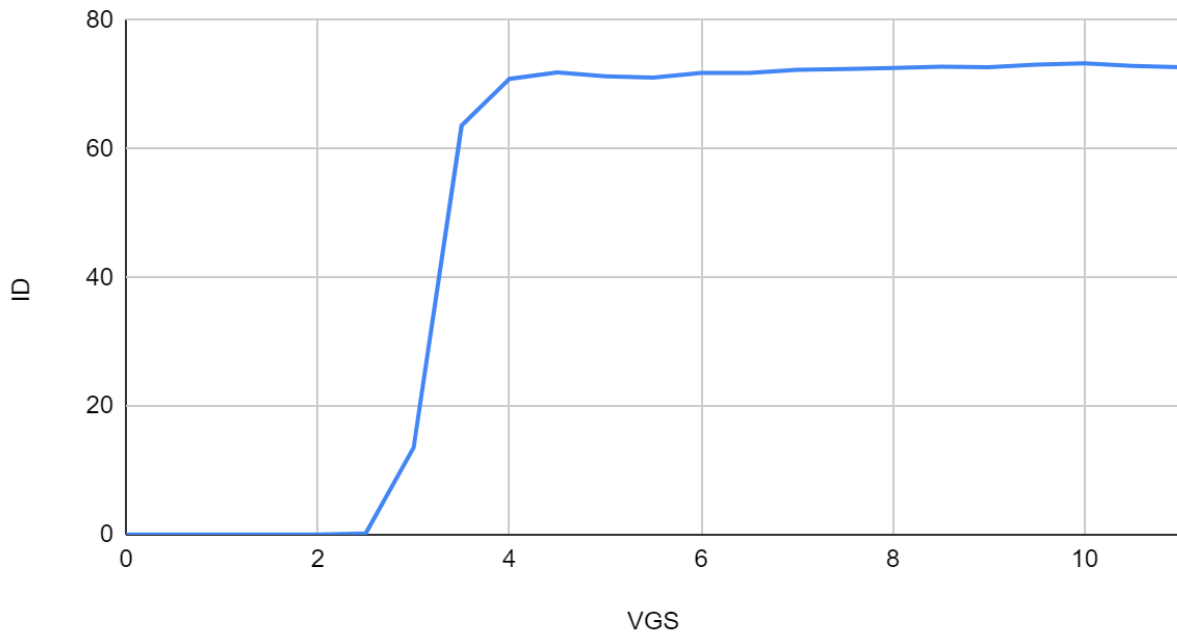

ID vs. VGS for VDS= 11V

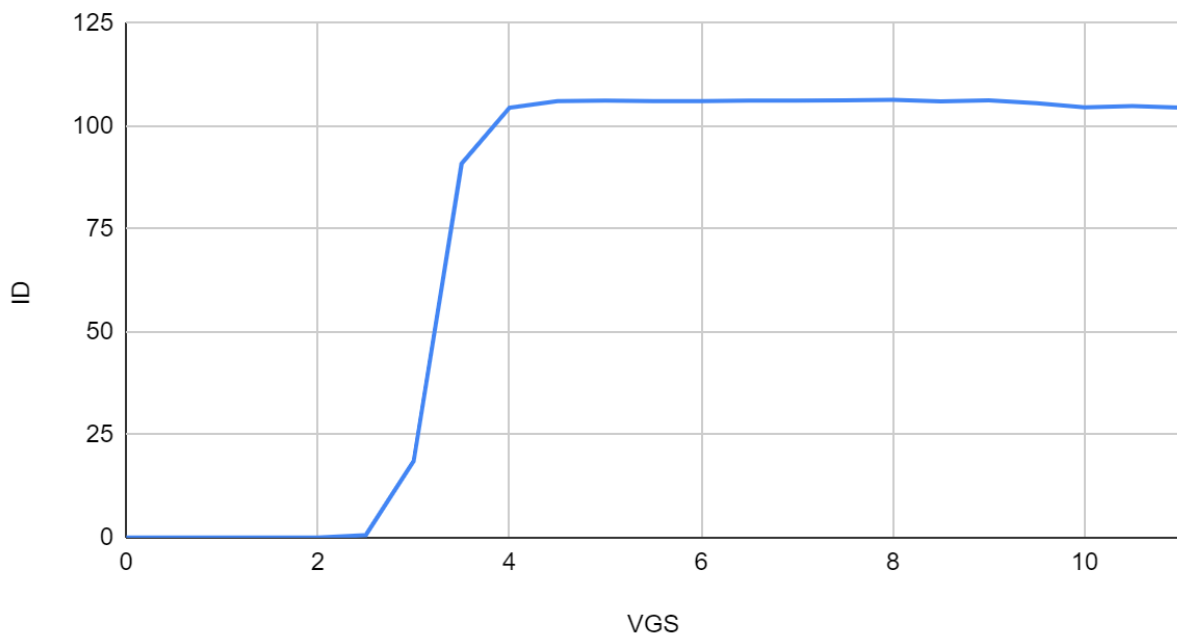

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

OUTPUT CHARACTERSTICS


V_{DS} (V)	$V_{GS} = 2.5\text{ V}$	$V_{GS} = 3\text{ V}$	$V_{GS} = 3.5\text{ V}$
	I_D (mA)	I_D (mA)	I_D (mA)
1	0.23	1.04	0.99
2	0.23	1.97	1.91
3	0.23	2.98	2.84
4	0.23	3.98	3.86
5	0.23	4.89	4.79
6	0.24	5.87	5.70
7	0.24	6.92	6.63
8	0.24	7.79	7.59
9	0.24	8.85	8.91
10	0.24	9.87	9.82
11	0.24	10.87	10.9
12	0.25	11.68	11.83
13	0.24	12.30	12.90
14	0.24	12.59	13.84
15	0.26	12.86	14.88
16	0.26	13.13	15.83
17	0.26	13.26	15.80

EECS Laboratory Experiment 8


Rita Abani 19244

Date : 27- 03 -2022

ID vs. VDS for VGS = 2.5V

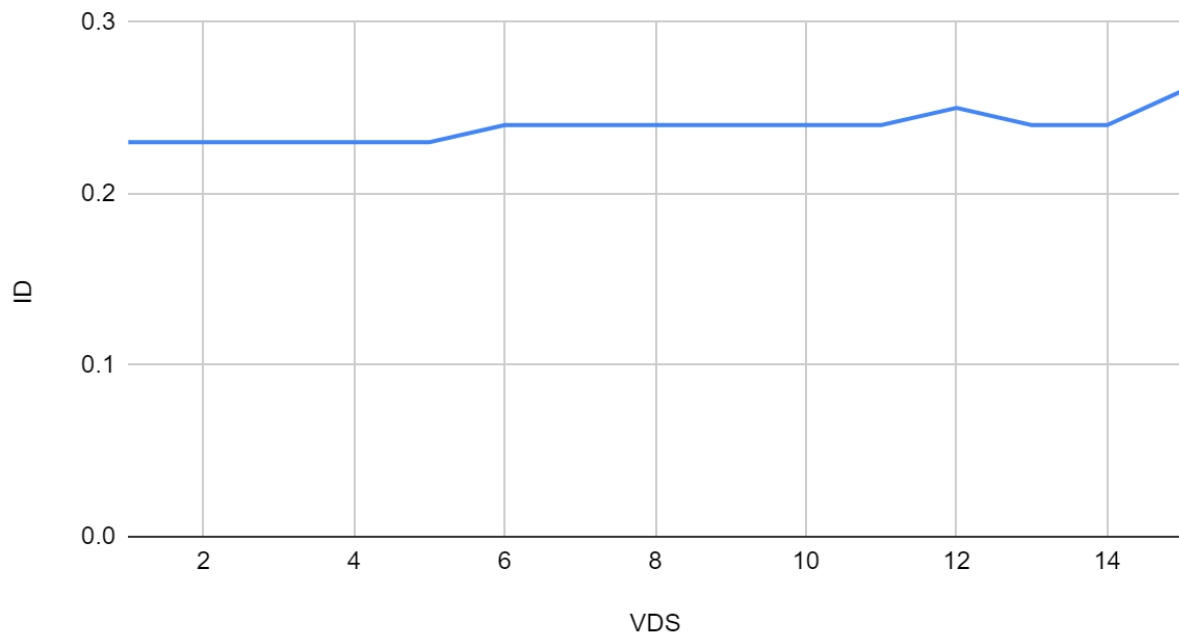


ID vs. VDS for VGS= 3V

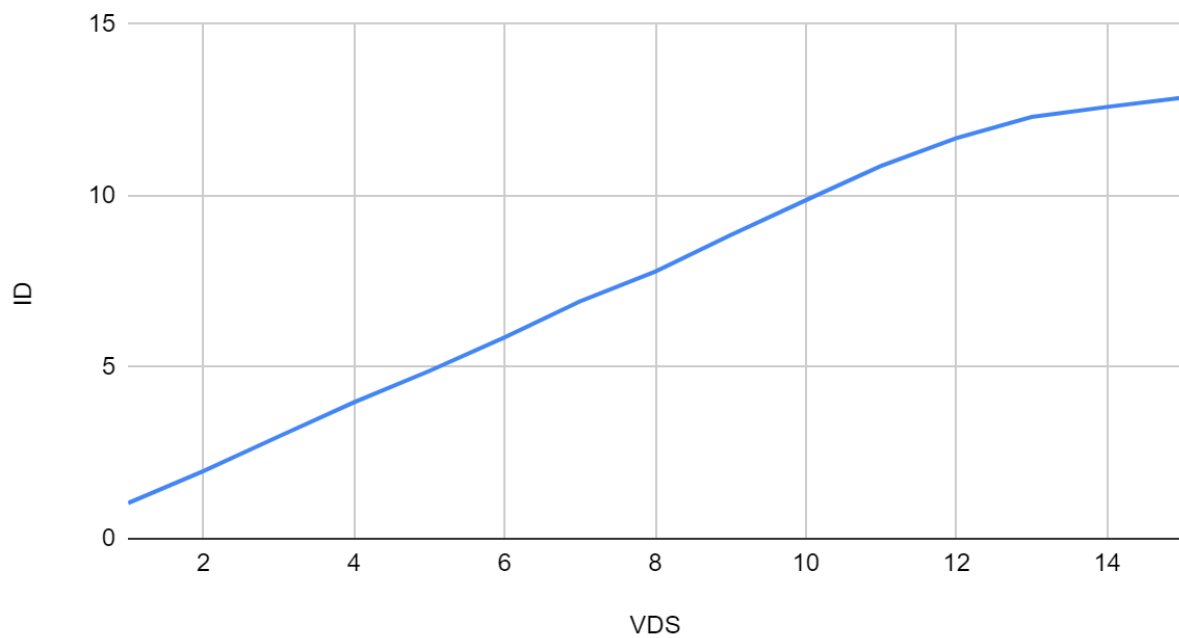

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

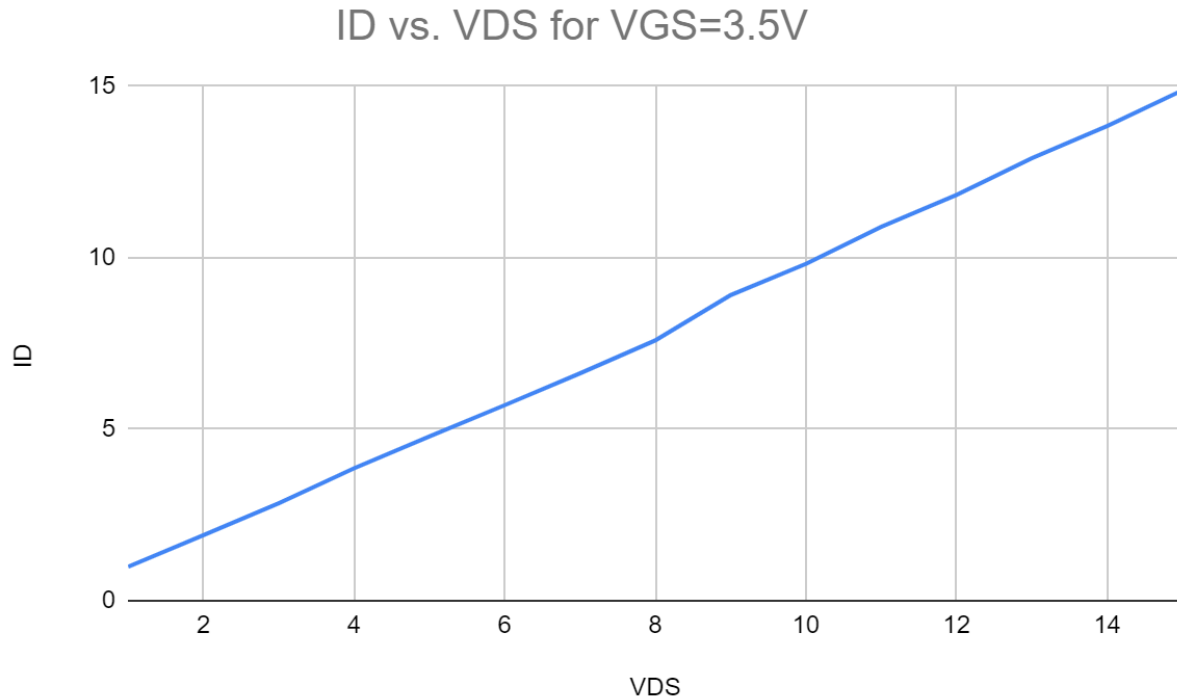

1. **Threshold voltage V_T :** Gate to source voltage at which, drain current starts flowing
2. **Transconductance g_m :** Ratio of small change in drain current (ΔI_D) to the corresponding change in gate to source voltage (ΔV_{GS}) for a constant V_{DS} .

$$g_m = \Delta I_D / \Delta V_{GS} \text{ when constant is } V_{DS}$$

3. **Output drain resistance:** It is given by the relation of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in Drain Current (ΔI_D) for a constant V_{GS} .

$$r_d \text{ or } r_o = \Delta V_{DS} / \Delta I_D \text{ at a constant } V_{GS}$$

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

RESULTS:

1. V_T : 0.5 V

2. g_m : approximately 1.75 mA/V (calculated graphically) for $V_{DS} = 8V$

1.925 mA/V (calculated graphically) for $V_{DS} = 11V$

Average $g_m = 1.8375$ mA/V

3. r_o : **45.5 k ohms for $V_{GS} = 2.5$ V**

0.8 k ohms for $V_{GS} = 3$ V

0.75 k ohms for $V_{GS} = 3.5$ V

Average $r_o = 47.05$ k ohms

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

For PMOS:



TRANSFER CHARACTERISTICS

V_{GS} (V)	$V_{DS} = 8\text{ V}$	$V_{DS} = 11\text{ V}$
	I_D (mA)	I_D (mA)
0	0	0
0.5	0	0
1	0	0
1.5	0	0
2	0	0
2.5	0	0
3	-0.02	-0.02
3.5	-4.58	-3.78
4	-7.69	-10.30
4.5	-7.70	-10.36
5	-7.71	-10.37
5.5	-7.71	-10.38
6	-7.71	-10.36
6.5	-7.70	-10.36
7	-7.72	-10.36

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

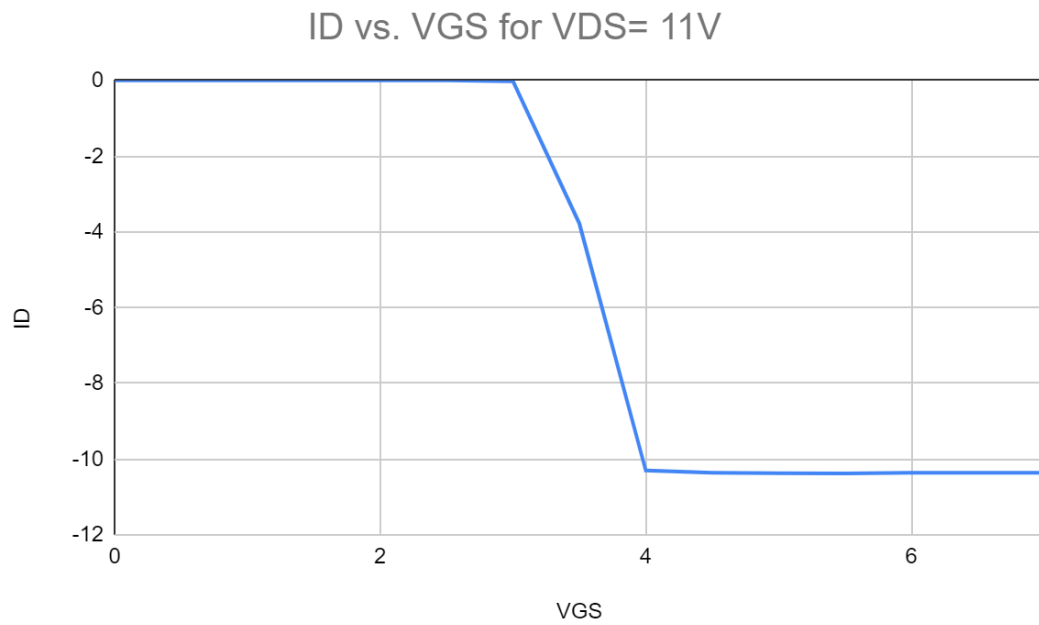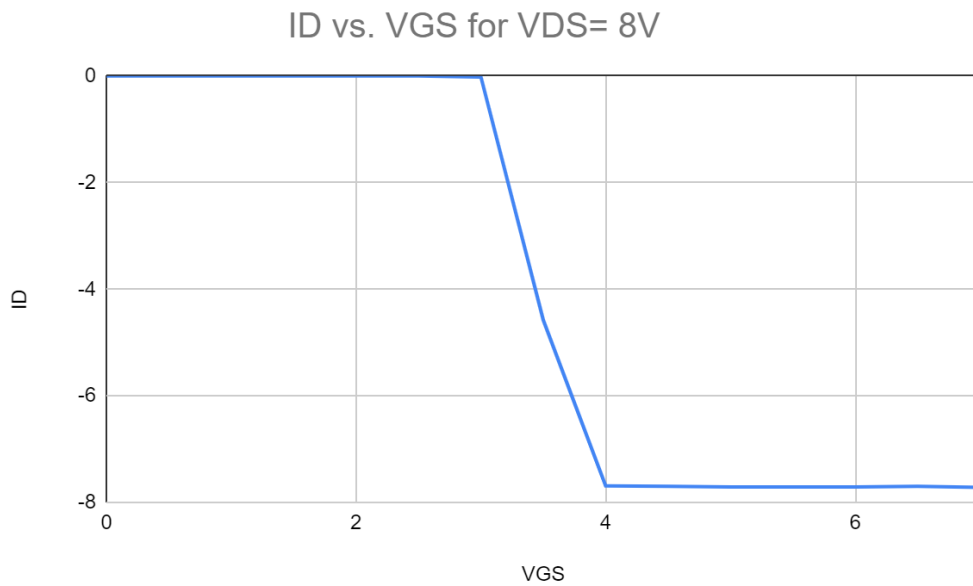

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022



OUTPUT CHARACTERISTICS

V_{DS} (V)	$V_{GS} = 3\text{ V}$	$V_{GS} = 3.5\text{ V}$	$V_{GS} = 4\text{ V}$
	I_D (mA)	I_D (mA)	I_D (mA)
1	-0.04	-0.94	-1
2	-0.04	-1.95	-1.81
3	-0.04	-2.92	-2.73
4	-0.04	-3.82	-3.22
5	-0.04	-4.73	-3.24
6	-0.03	-5.74	-3.24
7	-0.04	-6.61	-3.22
8	-0.04	-7.67	-3.22
9	-0.05	-8.61	-3.22
10	-0.04	-9.57	-3.22
11	-0.06	-10.40	-3.22
12	-0.06	-11.28	-3.22
13	-0.05	-12.24	-3.22
14	-0.05	-13.28	-3.24
15	-0.05	-14.23	-3.24
16	-0.05	-14.24	-3.24
17	-0.05	-14.24	-3.24

EECS Laboratory Experiment 8

Rita Abani 19244


Date : 27- 03 -2022

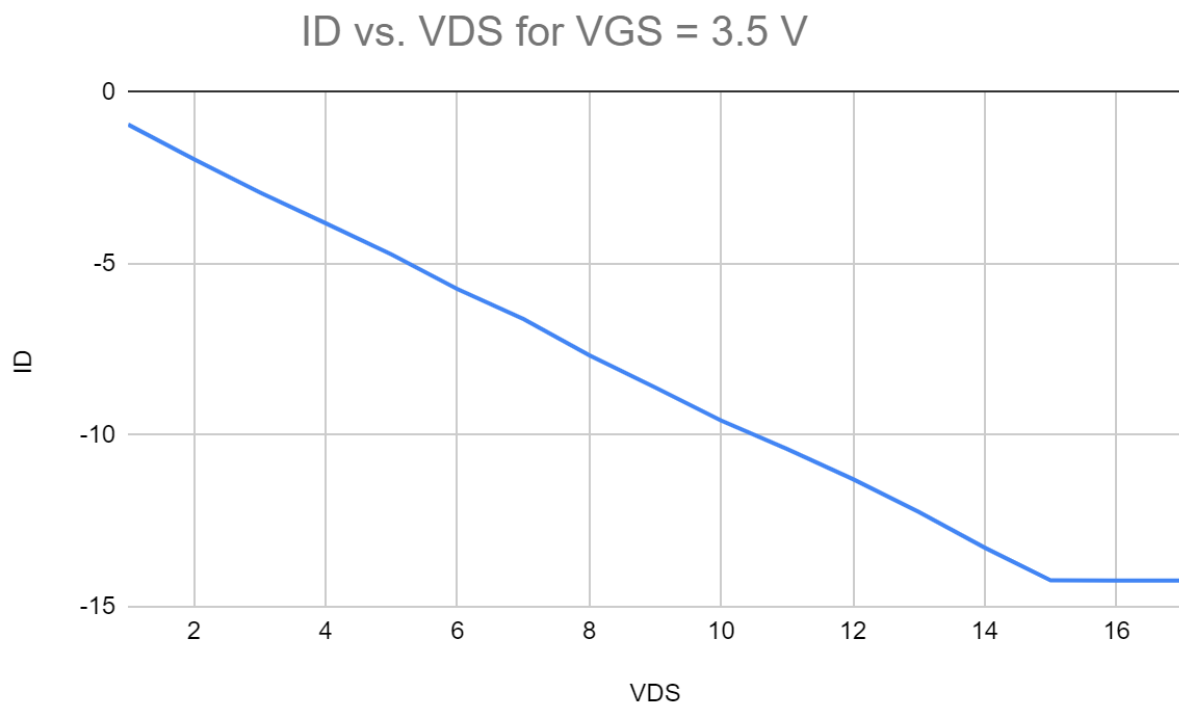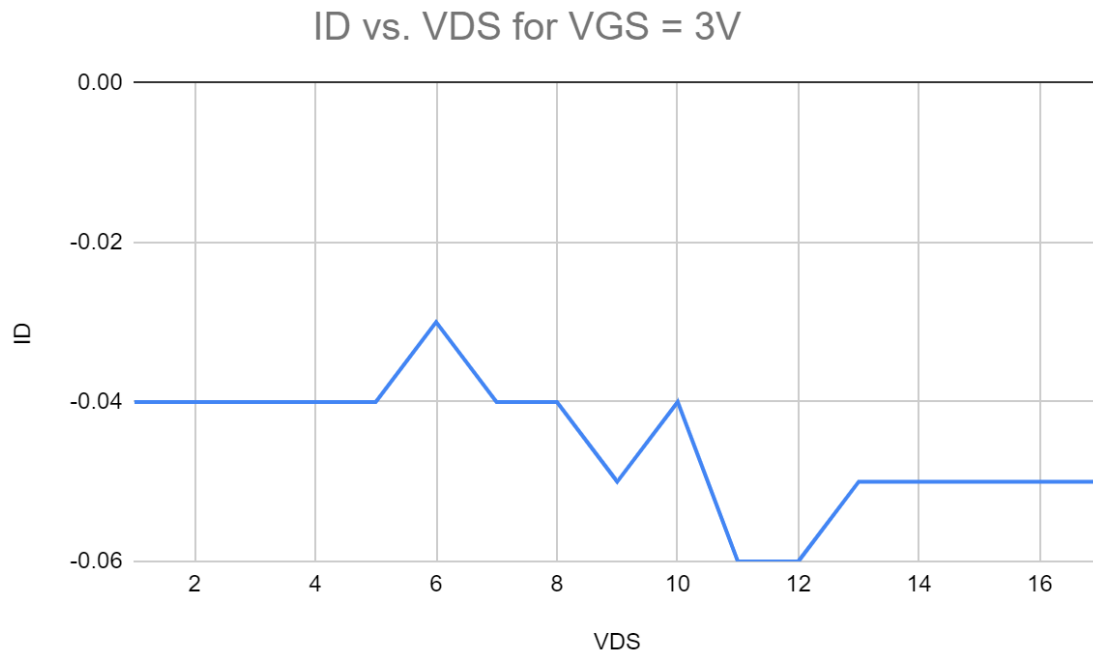

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

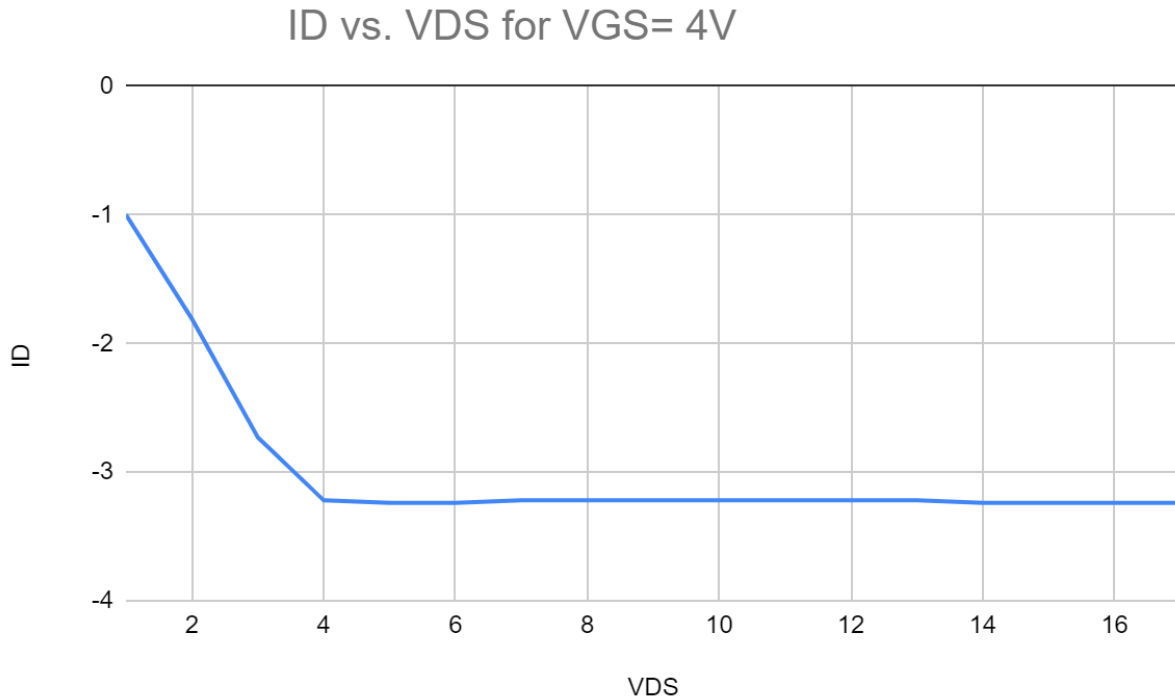

1. **Threshold voltage V_T :** Gate to source voltage at which, drain current starts flowing
2. **Transconductance g_m :** Ratio of small change in drain current (ΔI_D) to the corresponding change in gate to source voltage (ΔV_{GS}) for a constant V_{DS} .

$$g_m = \Delta I_D / \Delta V_{GS} \text{ when constant is } V_{DS}$$

3. **Output drain resistance:** It is given by the relation of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in Drain Current (ΔI_D) for a constant V_{GS} .

$$r_d \text{ or } r_o = \Delta V_{DS} / \Delta I_D \text{ at a constant } V_{GS}$$

RESULTS:

1. V_T : 3V
2. g_m : approximately 0.625 mA/V (calculated graphically) for $V_{DS} = 8V$

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022


7.52 mA/V (calculated graphically) for $V_{DS} = 11V$

Average $g_m = 4.0725 \text{ mA/V}$

3. r_o : 95.6 k ohms for $V_{GS} = 3 \text{ V}$
1.2 k ohms for $V_{GS} = 3.5 \text{ V}$
1.66 k ohms for $V_{GS} = 4 \text{ V}$

Average $r_o = 32.82 \text{ k ohms}$


CMOS inverter :

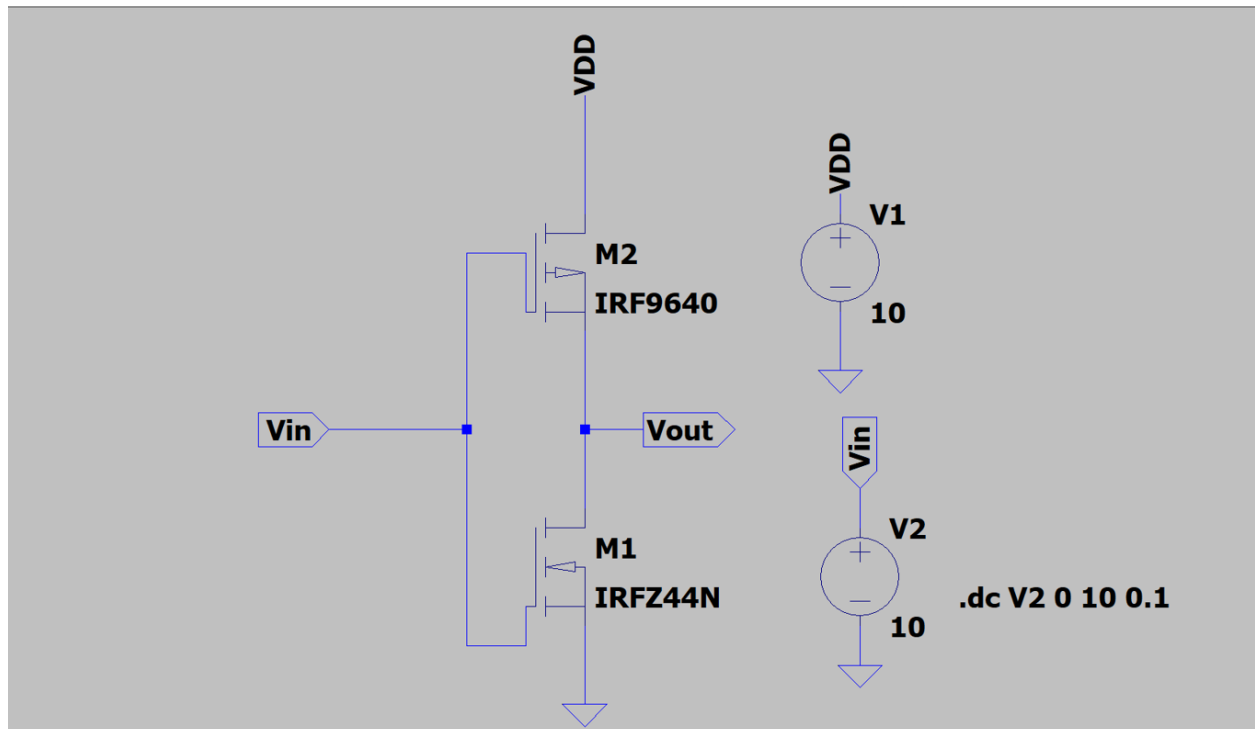

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

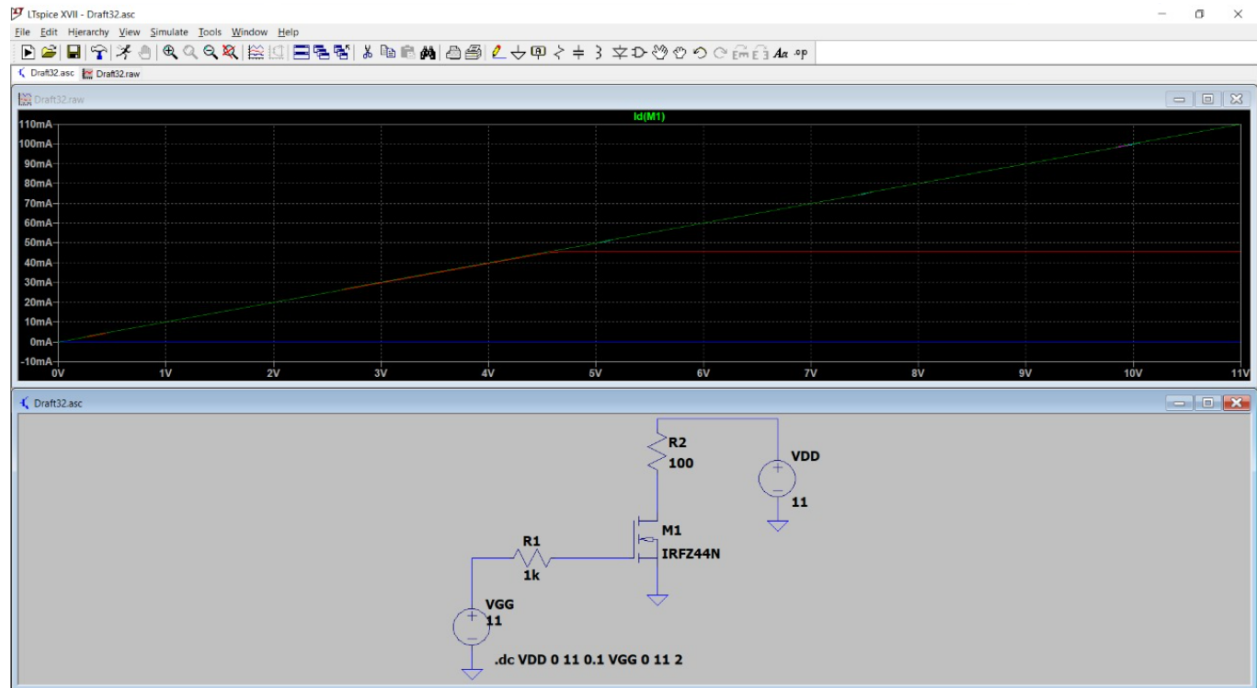

Vinput	Voutput
0	5.06
0.5	5.06
1	5.06
1.5	5.06
1.6	5.06
1.7	4.40
1.8	0.45
1.9	0.0062
2	0.0006
2.1	0.0002
2.2	0.0004
2.3	0.0002
2.4	0.0004
2.5	0.0003
2.6	0.0003
2.7	0.0003
2.8	0.0004
2.9	0.0004
3	0.0005
3.1	0.0006

EECS Laboratory Experiment 8

Rita Abani 19244

Date : 27- 03 -2022

3.2	0.0007
3.3	0.0007
3.4	0.0009
3.5	0.001
3.6	0.0012
3.7	0.0014
3.8	0.0017
3.9	0.0019
4	0.0021
4.5	0.0057
5	0.009
5.5	0.0134
6	0.0194

The voltage transfer characteristics are as follows :

